

Exam. Code: 0905
Sub. Code: 6952

1128
B.E. , First Semester
EC-101: Basic Electronics

Time allowed: 3 Hours

Max. Marks: 50

NOTE: Attempt five questions in all, selecting atleast two questions from each Unit.

x-x-x

UNIT - I

- I. a) With the help of suitable diagrams, differentiate between n-type and p-type extrinsic semiconductor materials.
b) How are semiconductor diodes used for rectification purpose? Explain the working of a half wave rectifier. (2x5)
- II. a) Describe the construction of an npn transistor.
b) Draw the output characteristics for a common-base transistor amplifier and explain its various regions. (2x5)
- III. a) Explain the enhancement mode of JFET along with its transfer curves.
b) What are some of the applications of MOSFETs? Explain any one in detail. (2x5)
- IV. Describe the application of an op-amp as a:
 - a) Phase shifter
 - b) Integrator
 (2x5)

UNIT - II

- V. a) How can a feedback circuit be used as an oscillator? Explain.
b) What is a weighted code? Give an example of a weighted and explain it. (2x5)
- VI. a) What are universal gates? How are they different from universal gates?
b) Give the characteristic tables of RS, D JK and T flip-flops. (2x5)
- VII. a) Design a full-adder and implement using logic gates.
b) Differentiate between decoders and demultiplexers. (2x5)
- VIII. a) What are transducers? List the different classification of transducers with examples each.
b) With the help of waveforms, differentiate AM, FM and PM. (2x5)

x-x-x