

Exam.Code:0927
Sub. Code: 6381

1078
B.E. (Electronics and Communication Engineering)
Third Semester
EC-318: Network Synthesis and Filter Design

Time allowed: 3 Hours

Max. Marks: 50

NOTE: Attempt five questions in all, including Question No. 1 which is compulsory and selecting two questions from each Section.

x-x-x

- I. (a) Define poles and zeros of a network function. What is their significance? (2)
- (b) List the properties of an ideal voltage source and ideal current source. (2)
- (c) Differentiate clearly between network analysis and network synthesis. (1)
- (d) What is a filter? (1)
- (e) Describe the concept of complex frequency. (2)
- (f) What is a symmetrical two port network? (1)
- (g) What is the use of network theorems in network theory? (1)

Section A

- II. (a) Define the elementary signals used in network analysis. (4)
- (b) State the necessary conditions for a network function to be transfer function for a one port passive network. (3)
- (c) State and explain Norton's theorem. (3)

- III. (a) In the circuit shown in figure 1, switch K is opened at $t = 0$ steady state conditions having been established earlier to the switching operation. Draw the transform network showing all initial conditions and hence find the current through the circuit for $t > 0$. (5)

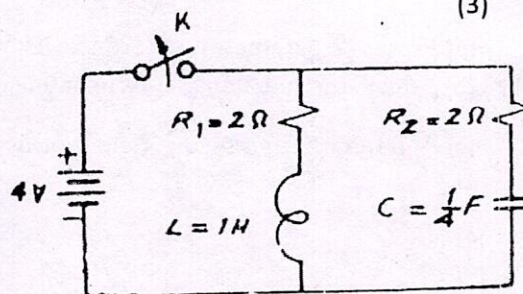


Figure 1

- (b) State Thevenin's theorem. Determine the Thevenin's equivalent circuit for the network shown in Fig 2. (5)

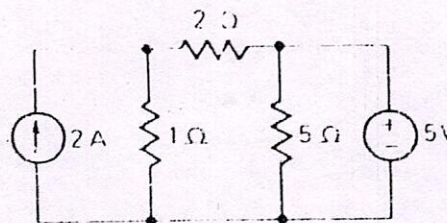


Figure 2

(a) Synthesize the network function $Z(s) = \frac{5s}{(s+1)(s+2)}$

(b) Obtain the function in time domain.
(c) Explain mesh analysis and node analysis with the help of example.

-2-

- IV. (a) A network function is given by: $Z(s) = \frac{5s}{(s+1)(s+2)}$. Draw the pole-zero plot and hence obtain the function in time domain. (5)
(b) Explain mesh analysis and node analysis with the help of example. (5)

Section B

- V. (a) Explain the concept of an ideal filter? Give classification of filters. (5)
(b) Design T and π -sections of m-derived high pass filter having cut-off frequency of 2 kHz and infinite attenuation frequency of 1.8 kHz and design impedance of 900 Ω . (5)

- VI. (a) Synthesize the network function $Z(s) = \frac{s(s^2+10)}{(s^2+4)(s^2+16)}$ in both Foster forms. (5)

(b) Define network parameters of a two-port network. Find the Z parameters for the network shown in figure 3. Also draw the equivalent circuit of the network in terms of these parameters. (5)

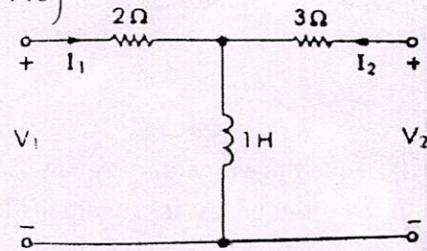


Figure 3

- VII. (a) Express Z-parameters in terms of its hybrid parameters for a two-port network. (2)
(b) Explain the function of a terminating half section in a composite filter. (3)
(c) Find the first and second Cauer forms of the network function $Z(s) = \frac{(s+1)(s+3)}{s(s+2)}$. (5)

x-x-x