

Exam.Code:0927
Sub. Code: 6896

1078
B.E. (Electronics and Communication Engineering)
Third Semester
EE-309: Electrical Science

Time allowed: 3 Hours

Max. Marks: 50


NOTE: Attempt five questions in all, including Question No. 1 which is compulsory and selecting two questions from each Part.

x-x-x

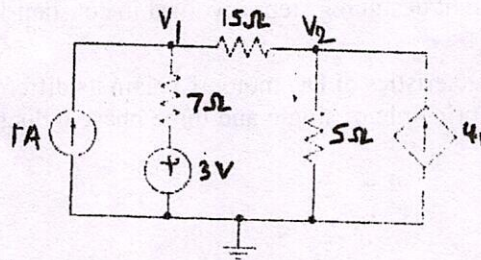- I. (a) Give one important basis to choose between nodal and mesh analysis of a circuit. (1)
- (b) A node where only two elements meet doesn't require a nodal equation. Why. (2)
- (c) Why RC timers are better choice than RL timers? (2)
- (d) How do you determine the current passing through independent voltage source? (2)
- (e) What are the differences between supermesh and supernode. (2)
- (f) A network has 5 branches and 2 independent loops. How many nodes are there in network? (1)


Part- A

- II.(a) Use superposition theorem to obtain the voltage across each current source in the given circuit diagram. (5)




- (b) What do you mean by duality principle? Explain with two examples. (5)

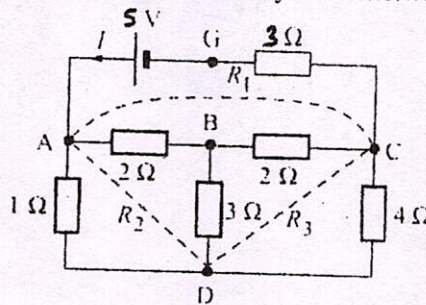- III. (a) Determine the current drawn from the 5-V battery in the network shown below. (5)



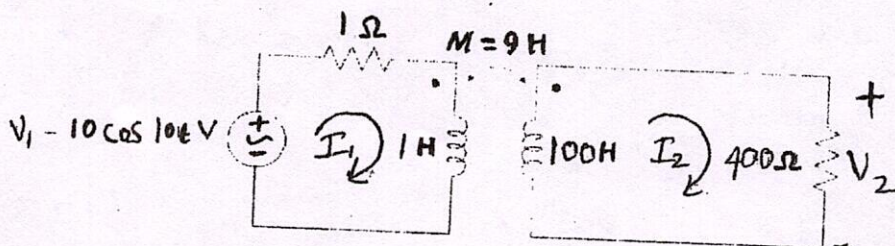- (b) For the circuit shown below, find the ratio of the output voltage across the 400Ω resistor to the Source voltage (5)




- IV. (a) What are the restrictions on pole-zero locations for any transfer function? Explain how location of poles and zeros affect the stability of network. (5)
(b) The current transfer function is given by (5)

$$I(s) = \frac{5s+3}{(s+2)(s^2+5s+2)}$$

Obtain its time domain response.

Part-B

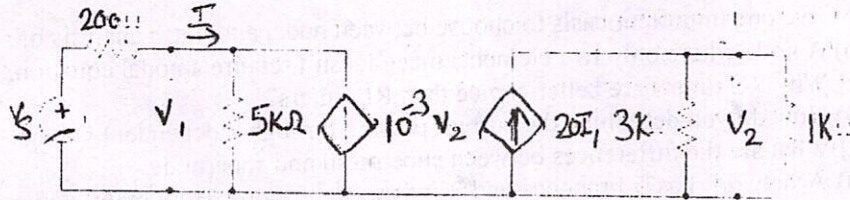- V. (a) Find y and z_{out} parameters for terminated two-port network shown below. (5)



- (b) Derive relation between y and T parameters for any two port networks. (5)
- VI. (a) What do you mean by characteristic impedance and propagation constant of pure reactive network. What are their significances? (5)
(b) What are the different designing steps involved in constant-k and m-derived filters. (5)
- VII. (a) What are the characteristics of DC motor. Explain its different types. (5)
(b) Explain working principle of single and three phase induction motors. Explain its torque-slip characteristics. (5)