

1078
B. Engg. (Electrical & Electronics Engg.)
3rd Semester
EE-305: Network Analysis and Synthesis

Time allowed: 3 Hours

Max. Marks: 50


NOTE: Attempt five questions in all, including Q. No. 1 which is compulsory and selecting atleast two questions from each Unit.

**_*_

- I. (a) Write STURM's test for PR functions.
- (b) What is the objective of using network theorems?
- (c) Name circuit elements of ac networks and classify them as active and passive elements.
- (d) Discuss significance of poles & zeros of a network.
- (e) Write significance of putting negative sign in port variables of transmission parameters. (5×2)


UNIT-I

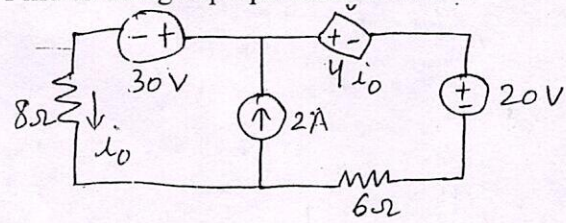- II. (a) Find to using superposition theorem:




- (b) Illustrate maximum power transfer with one example. (7+3)

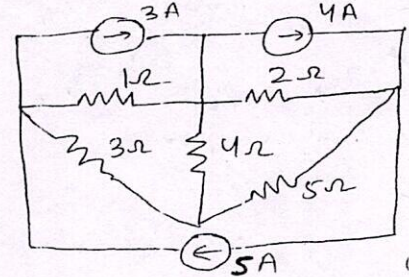- III. For the circuit shown, select a tree, determine branch voltages and branch currents using mesh current method.



(10)

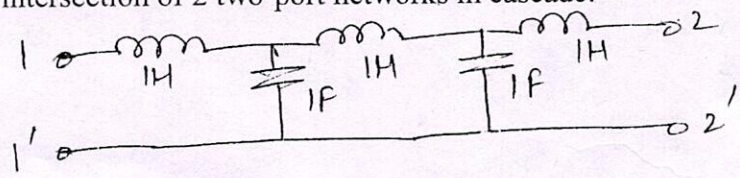- IV. Determine transmission parameters of the network shown using concept of intersection of 2 two-port networks in cascade:




P.T.O.

(2)

UNIT-II

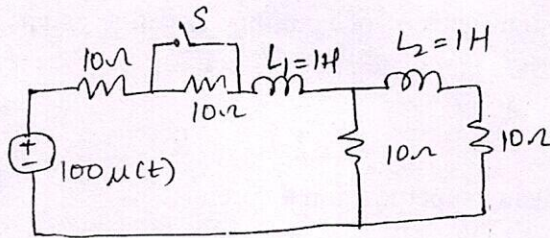- V. (a) Find the range of K for which the system will be stable:
 $s^3 + 10s^2 + (21+k)s + 13k = 0$
- (b) Discuss the necessary conditions for driving point function. (6+4)
- VI. Realise the following RC driving point function in: -
- (a) Foster-I form
- (b) Caver-I form $z(s) = \frac{s^2 + 6s + 8}{s^2 + 4s + 3}$ (5+5)
- VII. For the circuit shown, switch S is closed at $t=0$. Find current $i(t)$ for $t > 0$ through $L_2 = 1H$.



(10)
