

1058
B. Engg. (Electrical & Electronics Engg.)
6th Semester
EE-601: Computer Aided Power System Analysis
(May-2015)

Time allowed: 3 Hours

Max. Marks: 50

NOTE: Attempt five questions in all, including Q. No. 1 which is compulsory and selecting atleast two questions from each Unit.

-*-*-

- I. Attempt the following: -
- Why it is important to consider one bus as reference bus in load flow analysis?
 - What are the bolted faults?
 - How value of α in load flow analysis affects the convergence of a solution algorithm?
 - For a given n-bus system, what will be the size of z bus for s.c. studies.
 - What is meant by control area and ACE? (5×2)

UNIT-I

- II. (a) Draw the per unit circuit and determine the per unit impedances and per unit source voltage of the given circuit in Fig. 1. Use base value of 50MVA and 230 V in zone 1. Also calculate load current both in per unit and in amperes.


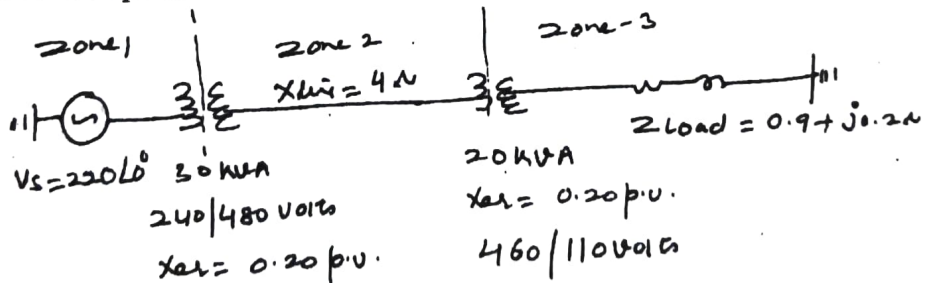


Fig.1

- (b) A power system operates an economic load dispatch with a system λ of 60 ₹/Mwh. If raising the O/P of plant-2 by 100 kw (while the other output is kept constant) results in increased power losses of 12kw for the system, what is the approximate additional Co st/hr if the output of this plant is increased by 2MW? (5+5)
- III. For the given system shown in Fig. 2, the reactive power limits for Bus-2 are $Q_{2min}=0$ and $Q_{2max}=0.8p.u.$ Update the voltage and phase angles using NR method perform one iteration. Neglect the charging admittances.

Contd....P/2

(2)

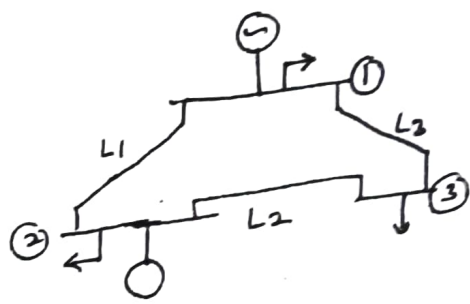

Line	Series impedance
L1	$0.025 + j0.1$
L2	$0.025 + j0.2$
L3	$0.025 + j0.1$

Fig 2

Bus No	Generation		Load		V _i
	P _{gi}	Q _{gi}	P _{oi}	Q _{oi}	
1	—	—	0.9	0.4	1.02
2	1.4	—	—	—	1.03
3	—	—	1.1	0.4	—

All values are in per unit. (10)

- IV. (a) Develop the block diagram of the LFC of a single area system.
 (b) Derive an expression for swing equation during transient state.
 (c) Find the critical fault clearing angle for clearing in fault with simultaneous opening of breakers CB₂ and CB₄. The generator is delivering 1.0 pu MW at instant preceding the fault. All the p.u. quantities on common MVA.

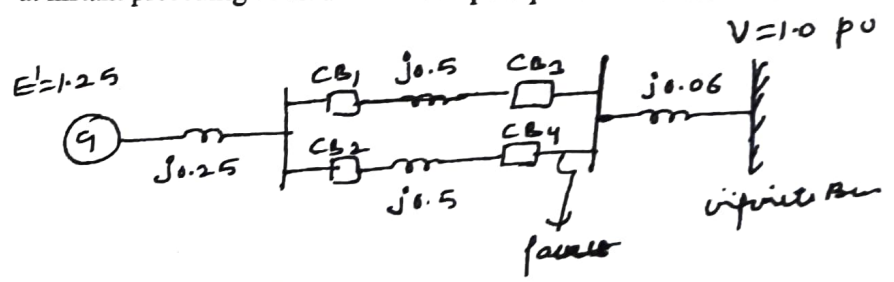


Fig. 3 (3+3+4)

UNIT-II

- V. A synchronous generator is supplying 60MVA power to a synchronous motor through a transmission line. All values are in p.u. computed on common basevalues of 100MVA, 11kv. The motor is drawing

(3)


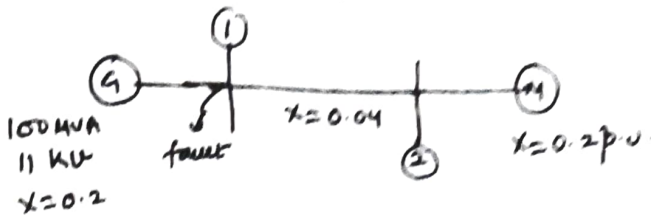


Fig. 4

50mw at 0.8pf (lead). Terminal voltage of motor is 10.9mv A 3 ϕ fault occurs at bus-1. Considering pre-fault load current, compute the total generator and motor currents under faulty conditions. (10)

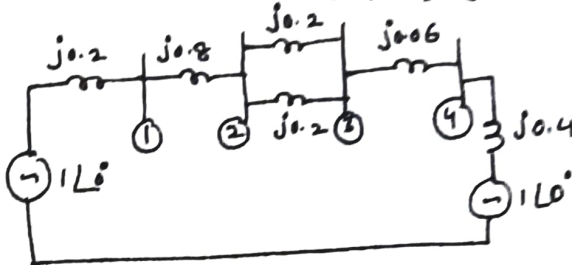- VI. (a) Prove that 3 ϕ complex power can be computed from symmetrical components of voltages and line currents of an unbalanced 3 ϕ circuit.
 (b) Obtain Z bus matrix using step-by-step algorithm.




All values are in p.u.

Fig. 5

(4+6)

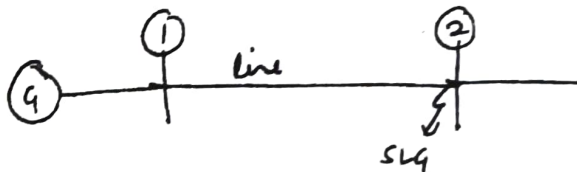- VII. (a) Derive an expression and draw sequence network for LLG fault in the presence of fault impedance on a synchronous m/c.
 (b) Determine in fault current magnitude if the generator natural is solidly grounded and $Z_f=0$; if the generator neutral is solidly grounded $Z_f=0.1$ pu on 40 MUA, 33kv if generator neutral is reactance grounded $X_n=0.1$ pu on 40MUA, 33kv, $Z_f=0$ pu. on 40 MUA, 33 kv. (5+5)



(5+5)
