

Exam.Code:0906
Sub. Code: 6680

1058
B.E. (Electrical and Electronics Engineering)
Second Semester
EE-E201: Electrical Measurement and Instrumentation

Time allowed: 3 Hours

Max. Marks: 50

NOTE: Attempt five questions in all, including Question No. 1 which is compulsory and selecting two questions from each Unit.

x-x-x

I. Attempt the following:-

- a) Give the difference between pointers and scales?
- b) Draw the basic potentiometer circuit?
- c) Write the general equation for bridge balancing?
- d) Draw and describe B H curve?
- e) Write the differences between PT and CT? (5x2)

UNIT - I

- II. What is standardization? Explain capacitance standard in detail. (10)
- III. Explain the operating principle of dynamometer wattmeter? (10)
- IV. Explain a potentiometer for measuring temperature through a thermocouple? (10)

UNIT -II

- V. The resistance of various arms of a wheatstone bridge are $P=2k\Omega$, $Q= 200 \Omega$, $R= 3000\Omega$ and $S = 150 \Omega$, If the battery emf is 8V and internal resistance is negligible, determine the sensitivity of bridge in terms of deflection per change in resistance. The galvanometer has current sensitivity of $10\text{mm}/\mu\text{A}$ and internal resistance of 100Ω . (10)
- VI. Obtain the expressions for balancing the Anderson bridge. Draw its phasor diagram also. (10)
- VII. Write a note on phase angle and ratio angle errors and about their minimization in instrument transformers. (10)

x-x-x