

Dec 2019

Exam.Code:0933
Sub. Code: 6973

1129
B.E. (Electrical and Electronics Engineering)
Third Semester
EE-305: Network Analysis and Synthesis

Time allowed: 3 Hours

Max. Marks: 50

NOTE: Attempt five questions in all, including Question No. 1 which is compulsory and selecting two questions from each Unit. Missing data (if any) can be appropriately assumed.

x-x-x

Q1. Explain briefly

- A) State the superposition theorem? Also write its limitations. (2)
- B) Differentiate between Planar and non planar graph with suitable example. (2)
- C) Write the generalized equations of two port network to find the T parameters. (2)
- D) Determine current transfer ratio $i_2(s)/i_1(s)$ for the network shown in fig. 1. (2)

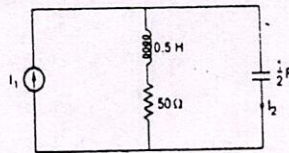


Fig. 1

- E) Write the necessary conditions to a polynomial to be Hurwitz. (2)

Part A

- Q2. A) Determine the voltages V_1 and V_2 in fig. 2. (5)

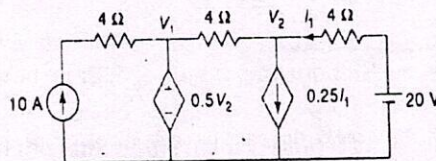


Fig.2

- B) A star connected load comprising two resistors and a pure inductor is connected to a symmetrical three phase supply voltage. If the numerical impedance of all branches is the same, find the voltage across each branch as a percentage of the line voltage. (5)

- Q3. A) For the network shown in fig. 3, assume elements between BC and BE as links, obtain f-cutest matrix. (3)

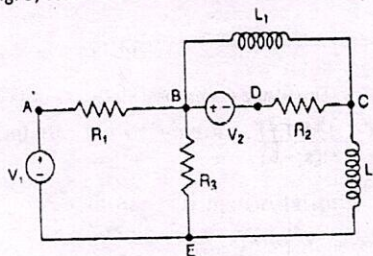


Fig. 3

- B) Obtain the incidence matrix, the node admittance matrix and the matrix node equation for the network shown in fig.4. (7)

P.T.O.

(2)

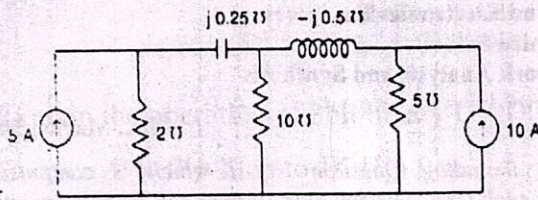


Fig. 4

Q4. A) The network of the fig. 5 is of the type used for the "Notch filter". For the element values given determine the y parameters. (5)

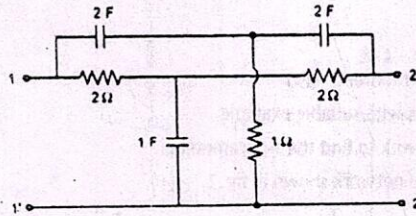


Fig.5

B) Derive the condition for the two port network to be symmetrical in terms of the Z parameters. (5)

Part B

Q5. A) The network shown in fig. 3 is in the steady state with switch K open. At t=0, the switch is closed. Find the expression for $V_2(t)$ for $t > 0$. (5)

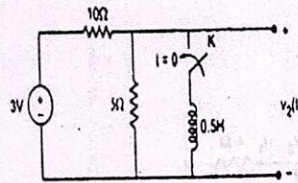


Fig. 6

B) Write the restrictions on poles and zeros for transfer function and driving point function. (5)

Q6. A) For the given function, draw pole-zero plot and hence obtain time domain response of voltage. (5)

$$V(s) = \frac{5(s+5)}{(s+2)(s+7)}$$

B) Use partial fractional expansion to determine the inverse Laplace transform of (5)

$$F(s) = \frac{5s+40}{s^2+12s+27}$$

Q7. A) Write all the properties of the LC driving point impedance function. (5)

B) Synthesize the function in R-L or R-C network using Cauer form -I and Cauer form -II. (5)

$$F(s) = \frac{2(s+1)(s+3)}{(s+2)(s+6)}$$

x-x-x