

1129
B.E. (Information Technology)
Third Semester
ITE-303: Digital Electronics

Time allowed: 3 Hours

Max. Marks: 50

NOTE: Attempt five questions in all, including Question No. 1 which is compulsory and selecting two questions from each Unit.

x-x-x

I. Answer the following:-

- a) Explain Demorgan's Law.
- b) What do you mean by terms "Fan-in" and "Fan-out"⁹
- c) What are the applications of Multiplexer?
- d) What is Race round condition? What is its solution?
- e) Compare PLA and PAL. (5x2)

UNIT - I

- II. A process is defined by the logical expression, $Z = AB + BC + CD + BD + BC$. Reduce the above expression to minimum no. of literals using:
 - a) Boolean algebra
 - b) K-map (2x5)
- III. What is a ring counter? What type of Flip-Flop is used in such counters? Write one application of this counter. (10)
- IV. Explain error correcting codes in detail. (10)

UNIT - II

- V. Write notes on following:-
 - a) ECL and DTL logic families
 - b) Shift Registers (2x5)
- VI. What is a dual slope A/D converter? Draw its circuit and explain its working. (10)
- VII. What is the difference between ROM and RAM? Draw the basic structure of RAM cell. Compare static and dynamic RAM cells. (10)

x-x-x