

1129
B.E. (Electronics and Communication Engineering)
Fifth Semester
EC-505: Digital System Design

Time allowed: 3 Hours

Max. Marks: 50

NOTE: Attempt five questions in all, including Question No. 1 which is compulsory and selecting two questions from each Unit.

x-x-x

- I. Attempt the following:-
 - a) What do you mean by canonical form?
 - b) How is a prime implicant chart reduced?
 - c) What are essential tests in fault detection?
 - d) What is terminal state in a finite state machine?
 - e) What is a merger table used for? (5x2)

UNIT - I

- II. a) Express the function $Y = A + B'C$ in canonical SOP and canonical POS form.
 b) Obtain the minimal SOP expression for the function using K-map:
 $Y = \sum m(1, 5, 7, 13, 14, 15, 17, 18, 21, 22, 25, 29) + \sum d(6, 9, 19, 23, 30)$ (10)
- III. Find the minimal sum of products for the following Boolean expression using the Quine-McCluskey method:
 $F(W,X,Y,Z) = \sum m(1, 3, 4, 5, 9, 10, 11) + \sum d(6, 8)$ (10)
- IV. Given the fault table shown below, where z denotes the fault-free output for the corresponding test:
 - a) Find the minimal set of tests to detect all single faults.
 - b) Find a preset set of tests to locate all single faults and show the corresponding fault dictionary.
 - c) Find a minimal adaptive fault-location experiment and compare the results with that of preset experiment.

Faults \ Tests	f1	f2	f3	f4	f5	z
T1			1	1	1	1
T2	1	1				0
T3				1	1	1
T4		1				0
T5					1	0

(10)
P.T.O.

(2)

UNIT - II

- V. a) Design a sequence detector that detects a sequence of 1011101 in the given binary input stream in non-overlapped manner.
- b) For the machine given below, find the equivalence partition and a corresponding reduced machine in standard form:

PS	NS, z	
	x = 0	x = 1
A	B, 0	E, 0
B	E, 0	D, 0
C	D, 1	A, 0
D	C, 1	E, 0
E	B, 0	D, 0

(2x5)

- VI. a) Design an asynchronous circuit that has two input inputs x_1 and x_2 and one single output z . The circuit is required to give an output whenever the input sequence 00, 10, 11 and 01 is received but only in that order.
- b) What do you mean by hazard free asynchronous sequential circuits? How can essential hazards be eliminated? (2x5)
- VII. Write short notes on:-
- a) Sequential machine flow charts
- b) Fault detection by path sensitizing (2x5)

x-x-x

Time
NOTI

I

II

IV

V