

Exam.Code:0906

Sub. Code: 6677

1019

B.E. (Computer Science and Engineering)

Second Semester

CS-203: Digital Electronics and Logic Design

Time allowed: 3 Hours

Max. Marks: 50

NOTE: Attempt five questions in all, including Question No. 1 which is compulsory and selecting two questions from each Unit.

x-x-x

I. Attempt the following:-

- a) Differentiate between encoder and decoder circuits.
- b) Explain universal gates. Design OR gate using NOR gates only.
- c) What are prime implicants and essential prime implicants?
- d) What are the applications of shift registers?
- e) Give difference between asynchronous and synchronous counters? (5x2)

UNIT – I

- II. a) Explain two input TTL NAND gate with suitable circuit diagrams.
b) Design and explain BCD to 7-segment decoder. (5,5)
- III. a) What is carry look-ahead adder? Explain with the help of suitable circuit diagram.
b) What is MOS family? Draw and explain CMOS NOR gate circuit. (5,5)
- IV. Minimize the following using K-map and implement using minimum number of NAND gates only:
 $F = \pi M(1,5,8,11,13,14,17,21,23,27,31). d(4,7,18,30)$ (10)

UNIT – II

- V. a) Differentiate between SISO and SIPO shift registers.
b) Design 3-bit up/down synchronous counter using D flip-flops. (5,5)
- VI. a) What is the difference between latch and flip-flop? Explain J-K flip-flop with circuit diagram.
b) What is a comparator? Design 4-bit magnitude comparator. (5,5)

P.T.O.

(2)

VII. Write short notes on the following:-

- a) Ring and Johnson counters
- b) Multiplexer and Demultiplexer

(5,5)

x-x-x