

Exam.Code:0906

Sub. Code: 7032

1019

B.E. (Electronics and Communication Engineering)

Second Semester

EC-201: Analog Electronic Circuits – I

Time allowed: 3 Hours

Max. Marks: 50

NOTE: Attempt five questions in all, including Question No. 1 which is compulsory and selecting two questions from each Unit.

x-x-x

- I. Attempt the following:-
- Which transistor configurations are capable of providing both voltage and current gains?
 - Why is the transistor referred to as a bipolar junction device?
 - What happens to the h-parameters when the junction temperature of a transistor increases?
 - What are the advantages of JFETs over BJTs?
 - Mention two differences between JFETs and MOSFETs.
 - What is the need for cascading amplifiers?
 - What is the condition that decides the oscillator's output frequency?
 - Which is the most popular oscillator configuration for audio applications?
 - Why are heat sinks used in power transistors?
 - What are class C amplifiers?

(10x1)

UNIT – I

- II.
 - Explain the principle of operation of a PNP transistor in the active region.
 - Compare the common-base, common-emitter and common-collector configurations of a transistor.
- III.
 - Derive the mathematical expression to prove that the operating point in voltage-divider bias configuration is independent of transistor gain B.
 - Derive the expression for the stability factor $S(I_{co})$ for fixed-bias configuration.
- IV.
 - How can we determine the h-parameters of a transistor using its input and output characteristic curves?
 - With the help of neat diagram, describe the operation of N-channel depletion MOSFETs.

(5,5)

P.T.O.

(2)

UNIT - II

- V. a) Explain the effect of coupling and bypass capacitors on the low-frequency response of the transistor-based amplifier.
- b) What are cascode amplifiers? What are the advantages offered by the cascode amplifiers? (5,5)
- VI. a) How does the circuit configuration of an oscillator differ from that of an amplifier? What are the different constituents of an oscillator circuit?
- b) With the help of a basic circuit diagram, briefly describe the operation of a Colpitts oscillator. (5,5)
- VII. a) Derive an expression to prove that the maximum efficiency in the case of a class B amplifier is 78.5%. What assumptions are made in calculating the maximum theoretical efficiency?
- b) What are the advantages offered by class A transformer-coupled amplifier over a direct-coupled class A amplifier? (5,5)

x-x-x