

Exam.Code:0921
Sub. Code: 6835

1079

B.E. (Information Technology) Third Semester
ITE-374/343/303: Digital Electronics

Time allowed: 3 Hours

Max. Marks: 50

NOTE: Attempt five questions in all, including Question No. 1 which is compulsory and selecting two questions from each Unit.

x-x-x

I. Answer the following:-

- a) What is a full subtracter? Give its truth table.
- b) Draw the logic diagram for the logic function $Z = (A+B+C).D$
- c) What is difference between synchronous and ripple counter.
- d) Explain the function of PRESET and CLEAR in Flip-flop.
- e) Explain noise margin and advantages of CMOS.

UNIT – I

- II. How will you convert R-S flip flop into J-K Flip flop? Also discuss characteristic table of J-K Flip flop. (10)
- III. Design MOD-6 up-down counter using D flip-flops. (10)
- IV. Explain error detecting codes in detail. (10)

UNIT – II

- V. What is the difference between ROM and RAM? Draw the basic structure of RAM cell. Compare static and dynamic RAM cells. (10)
- VI. Give the classification of TTL. Explain the working of TTL NAND Gate. (10)
- VII. Explain the operation of successive approximation type of ADC. (10)

x-x-x