

1059
B.E. (Electronics and Communication Engineering)
Fourth Semester
EC-406: Analog Electronic Circuits

Time allowed: 3 Hours


Max. Marks: 50

NOTE: Attempt five questions in all, including Question No. 1 which is compulsory and selecting two questions from each Part.

x-x-x


I. Attempt the following:-

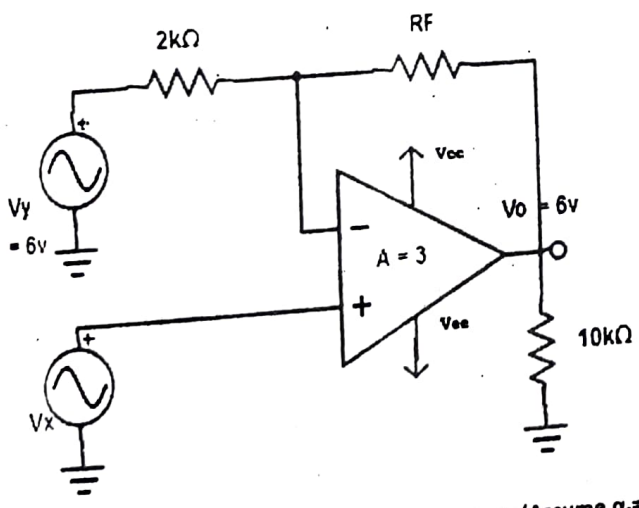- (a) Define slew rate and discuss its significance.
- (b) State the Barkhausen criterion for oscillation.
- (c) Show how a potentiometer can be connected to an op amp circuit so that the output dc offset can be adjusted to its minimum value.
- (d) For an op-amp differentiator with $R = 100\text{ K}\Omega$ and $C = 0.1\ \mu\text{F}$, an input of $2 \sin 1000 t$ is applied. Determine the value of v_o .
- (e) Give any limitation of using Op-amp as a Comparator.
- (f) What is thermal drift? How does it affect the performance of an op-amp circuit?
- (g) List applications of Transconductance amplifiers.
- (h) Calculate the current gain of Darlington Connection.
- (i) For the differential amplifier given below, Calculate V_o and R_f value.



(j) From the circuit, determine the output voltage (Assume $\alpha=1$)

(2)

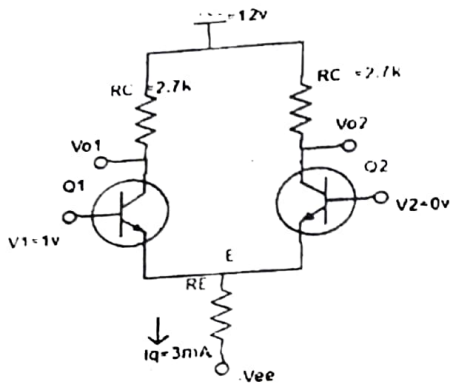

10

PART- A

- Q2. (a) What is a cascode amplifier? List the characteristics of the cascode amplifier. Draw equivalent circuit of cascode amplifier and calculate voltage gain, current gain and input resistance. 5
- (b) Design the dual-input balanced -output differential amplifier using the diode constant current bias to meet the following specifications:
- (a) Supply voltage $V_s = \pm 12\text{ V}$
 - (b) Emitter current I_e in each differential amplifier transistor = 1.5 mA. 5
 - (c) Voltage gain less than equal to 60. 5
- Q3. (a) Draw and discuss the hybrid π model for a transistor in CE configuration. 5
- (b) What are the characteristics of an ideal op-amp? List three open-loop op-amp configurations. Explain why open-loop op-amp configuration is not used in linear applications. 5
- Q4. (a) Briefly explain why negative feedback is desirable in amplifier applications? 5
- (b) In what way is the voltage follower a special case of the non inverting amplifier. 3
- (c) What is the need of Level Translator circuit? 2

PART- B

- Q5. (a) What is a frequency response? Briefly explain the need for compensating networks in op-amps. What is the difference between compensated and noncompensated op-amps? 5
- (b) Draw the high frequency equivalent circuit of an op amp. Explain in detail the major sources responsible for capacitive effect. Also evaluate the expression for output voltage gain as a function of frequency. 5
- Q6. (a) Design a first order high pass filter at a cut-off frequency of 400Hz and a pass band gain of 1. 5
- (b) Explain the difference between (a) inverting and differential summing amplifiers and (b) inverting and Noninverting averaging amplifiers. 5
- Q7. (a) Design a narrow band pass filter so that $f_c = 2\text{ KHz}$, $Q = 20$, $A_v = 10$. 5
- (b) What is the difference between clipper and clampers? Design a negative clipper circuit with reference voltage (i) +3V (ii) -3V 5