

Time allowed: 3 Hours

NOTE: Attempt five questions in all, including Question No. 1 which is compulsory and selecting two questions from each Part.



x-x-x

- 1.(a) What is doping? An intrinsic sample of Si is to be converted to an n-type extrinsic material. Which are the possible elements you would dope? (2)
- (b) Why does very small current flows through the p-n junction under reverse bias? (2)
- (c) Define common mode rejection ratio (CMRR). How does it influence the gain of a differential amplifier? (2)
- (d) What is difference between Latch and Flip-flop? (2)
- (e) What is modulation index? (2)

Part- A

2. (a) Give qualitative analysis of a P-N junction as a diode and draw its V-I characteristics and explain its temperature dependence. (5)
- (b) Differentiate between Intrinsic and Extrinsic semiconductors. (2)
- (c) Discuss the evolution of Electronic devices and Integrated circuits in brief. (3)

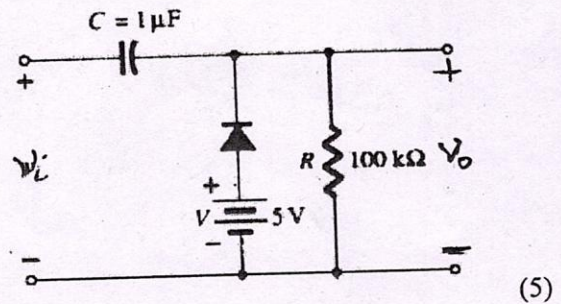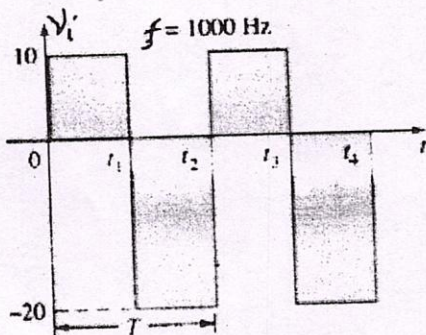3.(a) Determine output v_o from the circuit diagram shown below with respect to the input signal as indicated as v_i :



(b) Draw the circuit of transistor in the CE configuration, sketch the output characteristic & indicate active, saturation, & cutoff regions. (5)

4. (a) Perform following subtraction using 2's complement method. (2)
 $(11000)_2 - (11001)_2$

(b) Convert the following nos.

(i) $(58)_{10} = ()_2$

(ii) $(476)_8 = ()_{16}$

(iii) $(5C5)_{16} = ()_{10}$

(c) Reduce the following Boolean expression with the help of a Karnaugh's map and show its implementation using two input NAD gates only. (5)

$F(a,b,c,d) = \sum m(2,3,8,10,11,12,14,15)$

(2)

Part-B

- 5.(a) What is race around condition? Describe its possible solutions. (5)
(b) What are synchronous counters? Design a decade synchronous counter. (5)
- 6.(a) A 5-bit DAC has a current output. For a digital input of 101000, an output current of 10mA is produced. What will I_{OUT} be for a digital input of 11101? (3)
(b) What do you know about quantization error? (2)
- (b) What is OPAMP? Discuss the application of an OP-AMP as summing amplifier and difference amplifier. (5)
- 7.(a) Give the details of various frequency bands for communication. (3)
(b) What is modulation? (2)
(c) Give brief comparison of analog and digital communication systems. (5)

x-x-x