

2122
B. E. (Information Technology)
Third Semester
ESC-301: Digital Electronics

Time allowed: 3 Hours

Max. Marks: 50

NOTE: Attempt five questions in all, including Question No. 1 which is compulsory and selecting two questions from each Part.

x-x-x

1. a) Write down disadvantages of Analog Signals.
- b) What are applications of Grey Codes?
- c) Define following parameters:
i) Fan-in ii) Power Dissipation
- d) Define redundant group in K-map.
- e) Write various types of ROMs. (5*2=10)

Part-A

2. a) Apply Demorgan's theorem to the following expression:
$$\overline{AB} (CD + \overline{EF}) . (\overline{AB} + \overline{CD})$$

b) Using Boolean Algebra show that
$$(A+B) (\overline{A}+C) (B+C) = AC + \overline{BA}$$
 (2*5=10)
3. a) Explain the triggering methods of latches and flip-flops in detail.
b) What is Race around Condition? How can be it avoided? (2*5=10)
4. Design a synchronous counter using J-K flip-flop to count the following states only:
1,2,3,1,2,..... (10)

Part-B

5. a) Write down the drawbacks of Binary Weighted Resistance D/A converters.
b) What are the advantages of the R-2R ladder DAC over the weighted resistor type DAC? (2*5=10)
6. Explain the various characteristics of logic families in the detail. (10)
7. Explain the classifications of memories and their characteristics in the detail. (10)

x-x-x