

2122

B.E. (Electronics and Communication Engineering)

Fifth Semester

EC-505: Digital System Design

Time allowed: 3 Hours

Max. Marks: 50

NOTE: Attempt five questions in all, including Question No. 1 which is compulsory and selecting two questions from each Part.

x-x-x

1

- What are multi output functions? Explain with an example. (2)
- Explain state assignment with the help of an example. (2)
- Explain block parity method for error detection and correction. (2)
- Explain stuck-at-zero and stuck-at-one faults. (2)
- What is the difference between critical and non-critical races? (2)

Part A

- 2 (a) Calculate the essential prime implicants for the following using Q-M method:
 $Y = \sum m (0,2,4,7,8,16,24,32,36,40,48)$ (5)

- (b) Minimize the following using K-map:

$$Y(A,B,C,D) = \prod M (1,2,3,8,9,10,11,14) \cdot d (7,15)$$

Also implement the circuit using NOR gates only. (5)

- 3 (a) Implement the following function $Y(A,B,C) = \sum m (0,1,3,5,7)$ using:

- Type 0 Mux designing
- Type 1 Mux designing
- Type 2 Mux designing. (5)

- (b) Explain error detection and correction techniques. (5)

- 4 (a) Explain path sensitizing method for fault detection in combinational circuits. (5)

- (b) Assume data 1001101 as number of message bits or data bits without parity bits. Check the error if any and find the correct code using Hamming codes. (5)

Part B

- 5 (a) Derive the state table and state diagram for the following

$$JA = XB', KA = 1, JB = X'A', KB = 1 \text{ and output } Y = B' + X' + A'$$

Also specify the type of clocked sequential circuit. (5)


- (b) Convert SR flip-flop to D flip-flop. (5)

- 6 (a) How hazards can be removed? Also explain cycles and hazards in asynchronous circuits. (5)

- (b) What are Moore and Mealy machines? Compare the machines with the help of suitable circuit diagram. (5)

- 7 (a) Write all the methods for fault detection in sequential circuits. Explain any one with suitable example. (5)

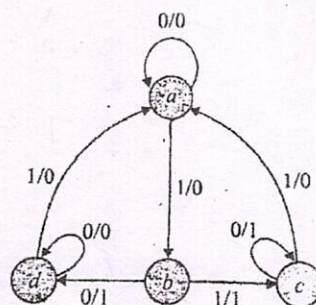- (b) Design a circuit that will function according to the given state diagram



(5)

x-x-x