

2072
B.E. (Electrical and Electronics Engineering)
First Semester
EE-E 101: Basic Electrical Engineering

Time allowed: 3 Hours

Max. Marks: 50


NOTE: Attempt five questions in all, including Question No. 1 which is compulsory and selecting two questions from each Unit.

x-x-x

- I. Attempt the following:-
- Define self and mutual inductance in electrical circuits. What do you mean by coefficient of coupling?
 - State and prove superposition theorem with the help of suitable example.
 - Write the application of D.C. series, shunt and compound motor.
 - The knowledge of phase sequence is very important in industries and power system. Why?
 - While performing short circuit test, rated voltage is never applied to the transformer, why?
- (5x2)

UNIT - I

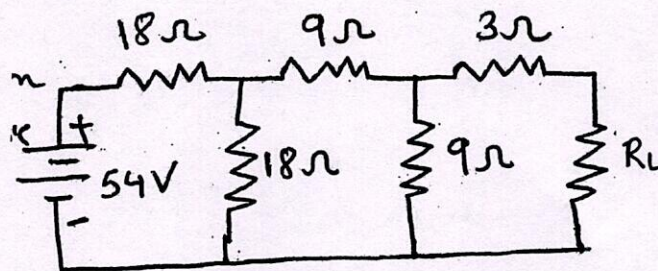- II. For the network shown in figure below:-



Determine the current flowing through R_L when the value of load resistant is

- 3 ohm
 - 6 ohm
 - 9 ohm
- (10)
- III. a) Explain why the phasor of voltage across an inductor leads its current by 90° and the phasor of voltage across a capacitor lags its current by 90° .
- b) A coil of resistance 15 ohms and inductance 0.05 Henry is connected in parallel with a non-inductive resistor of 20 ohms. Find current in each branch, total current supplied, phase angle of combination when voltage 230V at 50 Hz is applied. Draw relevant phasor diagram. (2x5)
- IV. a) How is power factor of a 3-phase balanced load can be determined using two-wattmeters?
- b) A 3- ϕ , 500 V motor load has a power factor of 0.4. Two wattmeters connected to measure power show the input as 30kW. Find reading in each wattmeter. (2x5)

P.T.O.

UNIT - II

- V. Does a magnetic circuit consume energy? Explain why? In a magnetic material hysteresis loss can not be reduced to zero, why? Also make a comparison between electric and magnetic circuits. (10)
- VI. a) Define efficiency of a transformer and find the condition for obtaining maximum efficiency.
- b) Calculate value of voltage regulation at 0.8 p.f. lagging for a transformer with resistance drop 2% and reactance drop 4% of the voltage. (2x5)
- VII. Write note on the following:-
- a) Single line diagram of distribution network
- b) Operating principle of 3- ϕ induction motor (2x5)

x-x-x