

2072

M. Tech. (Microelectronics)

Second Semester

MIC-204: Advanced Memory Technology and Design

Time allowed: 3 Hours

Max. Marks: 50

NOTE: Attempt five questions in all, including Question No. 1 which is compulsory and selecting two questions from each Section.

x-x-x

1. a) Write note on Hot-electron Injection. (5x2)
- b) What are Design Approaches in memory chip design?
- c) Explain Redundancy techniques.
- d) Explain the On-chip testing Scheme.
- e) Explain the operation of DRAM cell.

Section A

2. a) Explain the basic operation of 1-T cell. (5)
- b) Explain the basic functioning of flash memory cells with diagram. (5)
3. Draw and explain all the composition of basic memory circuit. (10)
4. Describe the role of V_{BB} generator and reasons why its needed. (10)

Section B

- 5.a). Explain the basic chip configuration and operation of DRAM chip with diagram. (5)
- b). What is Address Multiplexing and its basic operation. (5)
6. Explain the following with diagram:
 - a). The address buffer
 - b). Multi-divided data line
 - c). Refresh-Relevant Circuits. (3+3+4)
7. Explain the Standard DRAM with block diagram and also explain its read-write cycle. (10)

x-x-x