

2123
B.E. (Electrical and Electronics Engineering)
Third Semester
PC-EE-303: Analog Electronics

Time allowed: 3 Hours

Max. Marks: 50

NOTE: Attempt five questions in all, including Question No. 1 which is compulsory and selecting two questions from each Unit.

x-x-x

I. Attempt the following:-

- a) How ideal diode works as a switch. Plot its VI characteristics.
- b) Why common collector can be used as a buffer amplifier? List two other applications.
- c) Which configuration of MOSFET has infinite input resistance and low voltage gain?
- d) Why FETs are called as voltage controlled devices and BJTs as current controlled devices.
- e) If two inputs to a differential amplifier is 150 and $140\mu\text{V}$, calculate output voltage if gain is 2000. (5x2)

UNIT - I

- II. a) Find $V_{dc}(\text{out})$ for a HWR if the rms value of voltage is 110V at 50Hz and its turns ratio is 10:1. Consider use of silicon diode. .
b) A FWR is fed from a transformer with centre tapped secondary winding. The rms voltage from either end of secondary to centre tap is 50V. If the forward resistance of diode is $15\ \Omega$ and secondary winding resistance is $20\ \Omega$ and load resistance is $500\ \Omega$, calculate the ripple factor and the efficiency. (10)
- III. Draw a h-parameter model for a CE BJT amplifier. Calculate all the h parameters such as voltage gain, current gain, input impedance and output impedance for the CE model of transistor. (10)
- IV. Draw the drain and transfer characteristics for N channel MOSFET. Draw its symbolic representation and explain the parameters plotted in the graph. (10)

P.T.O.

(2)

UNIT - II

- V. What is the need of cascading in amplifiers? Draw a circuit of a differential amplifier in its best configuration and explain its working. What are the advantages and disadvantages of such amplifiers over other amplifiers? (10)
- VI. Calculate the input and output power for a power amplifier. The operating point is at 250mA, 8V and output current swings between 450mA and 40mA while output voltage is given from 15V to 1V. (10)
- VII. How op amp can be used as a hysteretic comparator. Plot its waveforms for positive and negative reference voltages. Also explain a circuit which will be formed when the reference voltage will be 0V. (10)

x-x-x