

Exam.Code:0933

Sub. Code: 6659

2123

B.E. (Electrical and Electronics Engineering)

Third Semester

PC-EE-304: Digital Electronics

Time allowed: 3 Hours

Max. Marks: 50

**NOTE:** Attempt five questions in all, including Question No. 1 which is compulsory and selecting two questions from each Unit.

x-x-x

I. Attempt the following:-

- a) How are negative numbers represented?
- b) Express the number  $2598.675_{10}$  in hexadecimal form.
- c) Explain the term Figure of Merit for a digital IC.
- d) What do you understand by Presettable Counters?
- e) What are the applications of a PLA? (5x2)

**UNIT - I**

- II. a) Design a Full Subtractor Circuit.  
b) Discuss an ADDER with Look-Ahead Carry (5,5)
- III. a) Design a 32:1 Multiplexer using two 16:1 multiplexers and one 2:1 multiplexer.  
b) Design a 2 bit Digital Comparator. (5,5)
- IV. a) Convert a SR flip flop to a D flip flop  
b) Explain design of a Bidirectional Shift Register. (6,4)

**UNIT - II**

- V. a) Design a 3-bit binary UP/DOWN counter with a direction control M. Use J K Flip Flops.  
b) Discuss the Successive Approximation A/D Converter. (5,5)
- VI. a) Describe ROM as a PLD.  
b) Explain briefly how to expand Word size and Word capacity for memory devices. (5,5)

P.T.O.

(2)

VII. Briefly describe any two of the following:-

- a) Johnson Counter
- b) Debounce Switch
- c) JK Master Slave Flip Flop

(2x5)

x-x-x