

2023
B.E.(Computer Science and Engineering),
First Semester
ESC-X06: Digital Electronics

Time allowed: 3 Hours

Max. Marks: 50

NOTE: Attempt five questions in all, including Question No. 1 which is compulsory and selecting two questions from each Unit.

x-x-x

I. Attempt the following:-

- a) Make a truth table for 3-input AND gate.
- b) What is a flip-flop? Give some of its applications.
- c) Give an example of PLA.
- d) Differentiate between bidirectional shift register and universal shift register.
- e) List two characteristics of ADC and DAC. (5x2)

UNIT - I

- II. Minimize the following expressions using K-maps and realize using NAND gates.
 $f_1(A, B, C, D, E) = \sum m (8, 9, 10, 11, 13, 15, 16, 18, 21, 24, 25, 26, 27, 30, 31)$ (10)
- III. Draw block diagram of a 1:64 demultiplexer tree and explain the principle of directing the input to the output. (10)
- IV. Write short notes on the following:-
 - a) Conversion of flip flops using excitation table.
 - b) Boolean Algebra (2x5)

UNIT - II

- V. What is dual slope A/D converter? Draw its circuit and explain its working. (10)
- VI. Design divide-by-5 ripple counter using FLIP-FLOPS. (10)
- VII. Write short notes on the following:-
 - a) Ring counter
 - b) Parallel in Parallel out shift register (2x5)

x-x-x