

2023

M. Tech. (Micro-Electronics)

First Semester

MIC-103: MOS Integrated Circuit Modeling

Time allowed: 3 Hours

Max. Marks: 50

NOTE: Attempt five questions in all, including Question No. 1 which is compulsory and selecting two questions from each Unit.

x-x-x

I. Attempt the following:-

- (a) Compare CMOS and bipolar technologies.
- (b) Why is NMOS technology more preferred than PMOS technology?
- (c) Define feature size and state the objectives of layout design rules.
- (d) What is body effect?
- (e) What is the purpose of a latch circuit? Draw one latch and explain. (5x2)

UNIT - I

- II. a) Explain the basic structure, operation and drain current characteristics of a depletion type MOSFET.
- b) Consider the following p-channel MOSFET process: Substrate doping $N_D = 10^{15} \text{ cm}^{-3}$, polysilicon gate doping density $N_D = 10^{20} \text{ cm}^{-3}$, gate oxide thickness $t_x = 650 \text{ \AA}$, and oxide-interface charge density $N_{ox} = 2 \times 10^{10} \text{ cm}^{-2}$. Use $\epsilon_{si} = 11.7\epsilon_0$ and $\epsilon_{ox} = 3.97\epsilon_0$ for the dielectric coefficients of silicon and silicon-dioxide, respectively, (i) Calculate the threshold voltage V_t , for $V_{SB} = 0$. (ii) Determine the type and the amount of channel ion implantation which are necessary to achieve a threshold voltage of $V_t = -2\text{V}$. (10)
- III. a) Discuss the Noise Margins for the CMOS Digital Integrated circuits with Help of logic families.
- b) Explain CMOS inverter with its equivalent circuit. (10)
- IV. a) Explain the different type of CMOS inverter switching.
- b) Explain in detail about RC delay estimation with suitable examples. (10)

P.T.O.

(2)

UNIT - II

- V. Sketch the logic gate symbolic representation of an JK Flip- flop using NAND gates. Give the truth table and describe the operation. Also sketch a CMOS circuit implementation. (10)
- VI. Write a short note on:-
(a) CMOS Transmission gate
(b) BICMOS Logic (10)
- VII. Draw a full adder circuit with CMOS logic and explain the functionality with help of Truth table. (10)

x-x-x