

2023  
B.E. (Electronics and Communication Engineering)  
Second Semester  
EC-204: Electrical Science

Time allowed: 3 Hours

Max. Marks: 50

NOTE: Attempt five questions in all, including Question No. I which is compulsory and selecting two questions from each Unit.

x-x-x

I. Attempt the following:

- a. What are different energy sources?
- b. Define the principle behind Reciprocity's Theorem.
- c. What is the relation between resistances of star and delta connections?
- d. How can the stability of network be defined using Routh-Hurwitz criterion?
- e. What is constant K type filter.

(5\*2)

UNIT-I

II. a. Find the equivalent star network of the circuit shown in fig. 1.

(5)

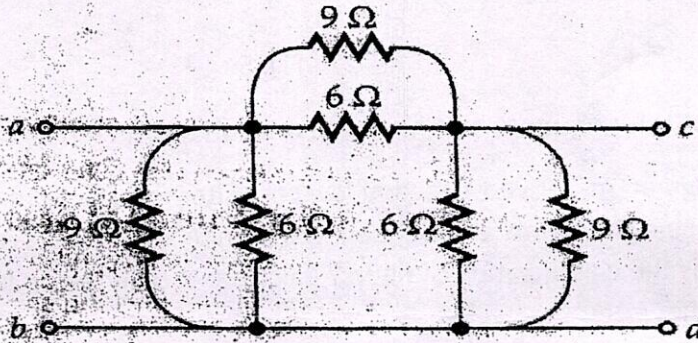


Fig.1

b. Find the current and power dissipated in the 5-ohm resistor in the circuit shown in fig.2.

(5)

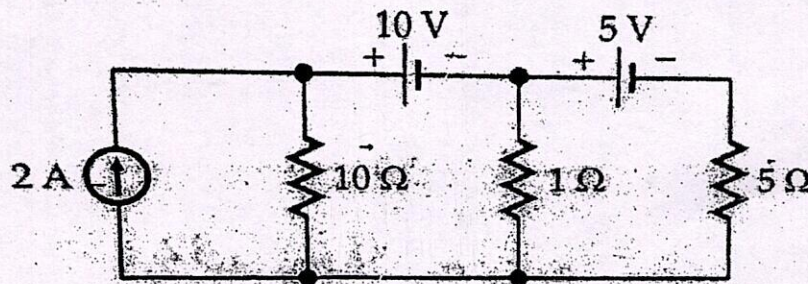


Fig.2

III. a. Explain Tellegen's Theorem with example.

(5)

b. What is the power loss in the 10-ohm resistor? Use Thevenin's theorem in fig. 3?

(5)

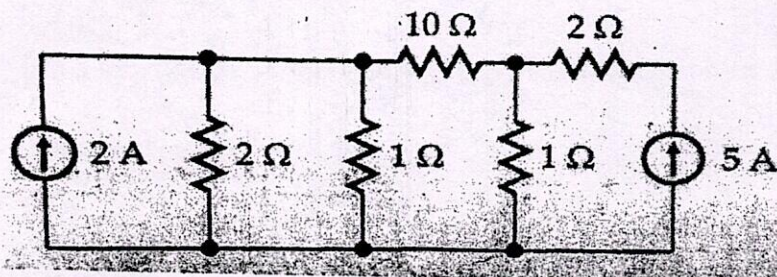


Fig. 3

(2)

- IV. a. Check the stability of the polynomial  $P(s) = S^6 + S^5 + 5S^4 + 3S^3 + 2S^2 - 4S - 8$  by applying Routh- Hurwitz criterion. (5)
- b. What are the restrictions on location of poles and zeros in driving point functions? (5)

UNIT-II

- V. a. Determine the Z-Parameters of the network shown in fig. 5. (5)

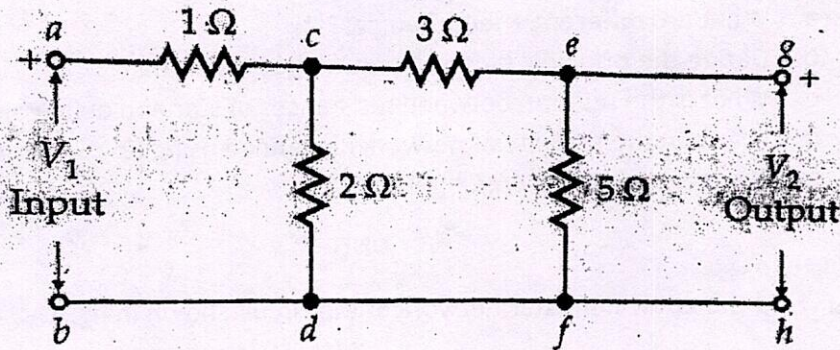


Fig. 5

- b. What is h-parameters. What is the relation between h and Z parameters? (5)
- VI. a. Design an m-derived T section low pass filter to have a cut-off at 7KHz and design impedance is 600 ohms and frequency of infinite attenuation is 10.5 KHz. (5)
- b. What is the classification of filters? Calculate the characteristic impedance for pure reactive network. (5)
- VII. a. On what principle single induction motor works. Write some applications. (5)
- b. What are different speed control methods for DC motor. (5)