

2023
B.E. (Electronics and Communication Engineering)
Sixth Semester
EC-625: Power Electronics

Time allowed: 3 Hours

Max. Marks: 50

NOTE: Attempt five questions in all, including Question No. 1 which is compulsory and selecting two questions from each Unit.

x-x-x

I. Answer in brief and to the point.

- a) What is Snubber circuit? Explain its working.
- b) What is meant by integrated cycle control?
- c) Why a PWM inverter is superior to a square wave Inverter? Discuss.
- d) In controlled rectifier, how will you ensure continuous load current? Describe.
- e) Why switching mode is used in power supplies? Give concept of soft-switching. (5x2)

UNIT - I

- II. a) What is power MOSFET? What are the types of power MOSFET? Write the difference between general purpose MOSFET and power MOSFET?
b) Describe the basic behavior of an SCR using a two-transistor model. (2x5)

- III. a) Draw and explain the working of a single-phase full bridge controlled rectifier with R and RL load and find dc output voltage.
b) A single phase fully controlled bridge converter with RL load is supplied from 220 V, 50 Hz ac supply. If the firing angle is 35° , determine
i) average output voltage
ii) output current
iii) input power factor (2x5)

- IV. a) What is the effect of source inductance in single -phase full - wave controlled bridge rectifier with RL load?
b) Draw the voltage and current waveforms. (2x5)

UNIT - II

- V. a) Explain the basic working principle of a 1-phase current source inverter.
b) Discuss the Principle of operation of forward and fly back converters in CCM. (2x5)
P.T.O.

(2)

VI. Write technical notes on the following:-

- a) Filters at the output of inverters
- b) UPS

(2x5)

VII. a) What types of disturbances are there on power lines? Discuss the role of power conditioner.

b) Discuss series loaded half bridge DC-DC converter.

(2x5)

x-x-x