

2063
M. Tech. (Microelectronics)
Second Semester
MIC-203: Analog and Mixed Signal Device Design

Time allowed: 3 Hours

Max. Marks: 50

NOTE: Attempt five questions in all, including Question No. 1 which is compulsory and selecting two questions from each Section.

x-x-x

1. Attempt all: (2*5)
- (a) Define the resolution, settling time and conversion time of D/A converters.
 - (b) Draw the circuit for analog multiplier.
 - (c) Write note on ADC architecture.
 - (d) Draw cascode amplifier configuration and list out its advantages.
 - (e) Explain the working and derive the output impedance of a simple MOS current mirror.

SECTION A

- 2. What is basic concept behind single stage amplifiers? Discuss about current source and sink of single stage amplifiers. (10)
- 3. Why diode connected load is important in common source stage. Derive an expression for small signal voltage gain for diode connected common source stage in MOSFET Technology. (10)
- 4. In fig. 1, Circuit uses a resistor rather than a current source to define a tail current of 1mA. Assume that $(W/L)_{1,2} = 25/0.5$, $\mu C_{ox} = 50 \mu A/V^2$, $V_{TH} = 0.6V$, $\lambda = \tau = 0$, and $V_{DD} = 3V$. (10)
 - (a) What is the required input Common Mode (CM) for which R_{SS} for which sustains 0.5V?
 - (b) Calculate R_D for a differential gain of 5.
 - (c) What happens at the output if the input CM level is 50mV higher than the value calculated in (a)?

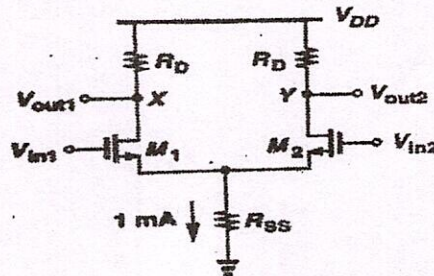


Fig.1

SECTION B

- 5. Discuss about single slope and dual slope ADC. (10)
- 6. (a) Differentiate between single ended and differential operation. Explain how input mode range is computed for a differential pair with diagram. (5)
 - (b) Discuss about Gilbert Cell. (5)
- 7. Derive mathematical expressions for differential gain and common mode gain of a differential pair in MOS Technology. (10)

x-x-x