

2063
B.E. (Electrical and Electronics Engineering)
Third Semester
ES-EE-301: Network Analysis and Synthesis

Time allowed: 3 Hours


Max. Marks: 50

NOTE: Attempt five questions in all, including Question No. 1 which is compulsory and selecting two questions from each Unit.

x-x-x

I. Attempt the following:-

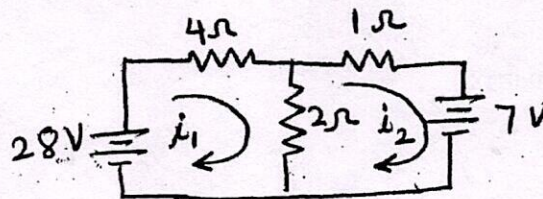a) Find the mesh currents of the circuit shown in figure:-



b) With an example, show how by applying Thevenin's theorem, current flowing through a branch of an electrical network can be calculated.

c) The impedance matrix of two part networks are given by $\begin{bmatrix} 3 & 2 \\ 2 & 3 \end{bmatrix}$ and $\begin{bmatrix} 15 & 5 \\ 5 & 25 \end{bmatrix}$.

If two networks are connected in series, what is impedance matrix of combination?


d) Bring out the significance of a Hurwitz polynomial in testing the positive realness of a function.

e) State the advantages offered by the graph theory as applied to electric circuit problems.

(5x2)


UNIT - I

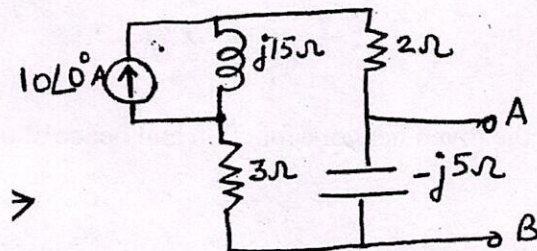II. Obtain Thevenin's equivalent circuit for the figure given as



(10)

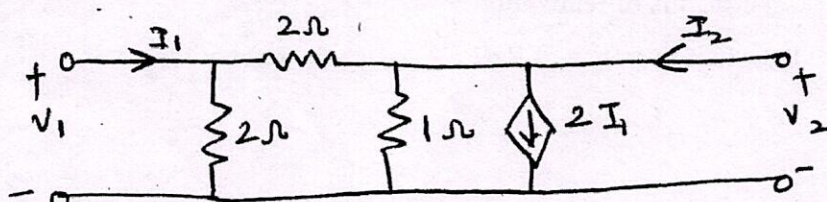III. Determine Y and Z parameters for the networks shown as




(10)

P.T.O.

(2)

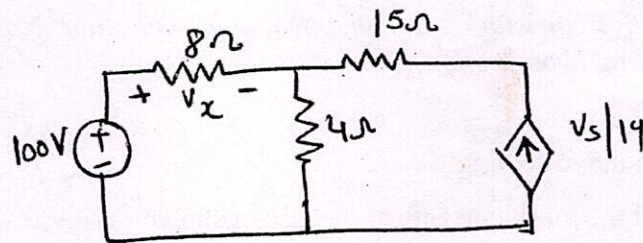IV. For the network shown in figure determine:-




- Tie-set matrix
- Loop impedance matrix
- Loop currents

(10)

UNIT - II

V. In the given circuit shown as

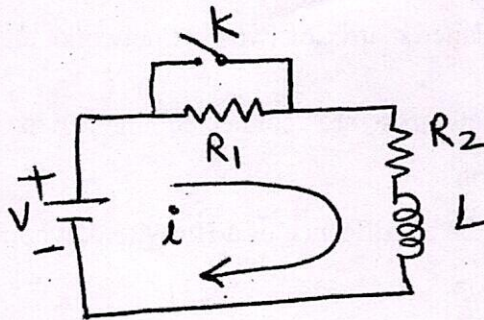

The switch k is closed at $t = 0$, the steady state condition reached. Obtain the expression for the current in the circuit at time t . If $R_1 = R_2 = 100\Omega$, $V = 10V$ and $L = 1H$. Calculate at $t = 5$ ms

- Current i
- Voltage across R_2

(10)

VI. Draw pole zero diagram for the given network function and hence obtain $v(t)$

$$V(s) = \frac{4(s+2)s}{(s+1)(s+3)} \quad (10)$$

VII. Write notes on the following:-

- Cauer forms of realization
- Transient response of R-C for sinusoidal excitation

(2x5)