

2063

B.E. (Electronics and Communication Engineering)

Fifth Semester

EC-505: Digital System Design


Time allowed: 3 Hours

Max. Marks: 50

NOTE: Attempt five questions in all, including Question No. 1 (Section-A) which is compulsory and selecting two questions each from Section B-C.

x-x-x

Section - A

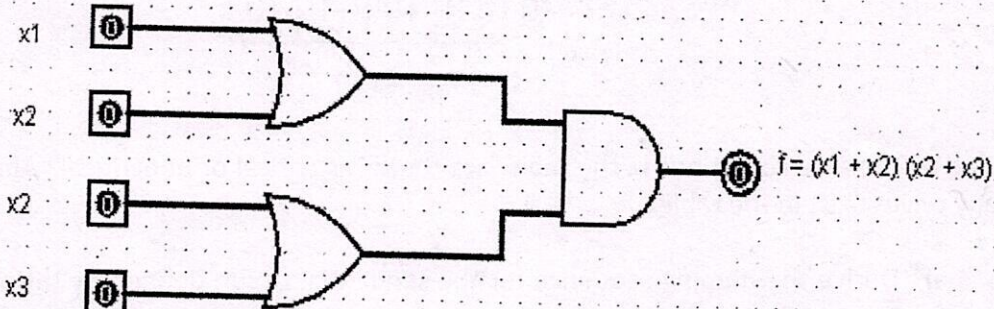1	a) Compare state diagram and state table. b) What is machine equivalence? Give an example. c) Differentiate between ASM chart and a conventional flow chart. d) What is hamming distance? Give an example. e) Differentiate combinational and sequential circuits.	10
Section-B (Attempt any two)		
2	a) Solve the following function using Q.M method. $Y = \sum_m(0,3,4,5,8,9,11,12,13,15) + d(1,2)$ b) Minimize and design the circuit using multiple output k-maps for $F1 = \sum_m(2,5,6,7,8,10,12,13,14,15)$, $F2 = \sum_m(5,8,9,10,11,12,13,14,15)$ and $F3 = \sum_m(2,6,7,9,11,13,15)$	5
3	a) Encode data bit 1101 into even parity hamming code. If received data is 1000101, then which bit encountered the error? b) Find the test-set for fault detection and location using fault table method for the circuit shown in Fig.1	5
	 <p style="text-align: center;">Fig.1</p>	5
4	a) Minimize the function $f(x_1, x_2, x_3, x_4) = x_1x_2x_3 + x_1x_2x_3 + x_1x_2x_3 + x_1x_3x_4$ using the iterative consensus method and also verify using iterative consensus tabular method. b) Find the Boolean difference of $F(X) = x_1x_2 + x_3$ with respect to x_2 using at least 4 methods.	5
Section-C (Attempt any two)		
5	a) Design a synchronous sequential circuit with one input line and with one output line that recognizes the input string $x = 1111$. The circuit is also required to recognize the overlapping sequences, as can be seen in the output string z that results from the following input strings $x = 1101111111010$, $z = 0000001111000$. b) Derive the minimal circuit for the sequential machine shown in fig. 2.	5

(2)

	x	
	0	1
A	B/1	D/0
B	-/-	B/0
C	E/0	D/-
D	B/1	A/0
E	-/-	C/1
F	-/0	E/1

Fig.2

6

- a) Design a pulse mode circuit with input x_1, x_2, x_3 and output z . The output must change from 0 to 1 if and only if the input sequence $x_1-x_2-x_3$ occurs while $z = 0$. The output must change from 1 to 0 only after an x_2 input occurs.
- b) Given the following excitation table shown in fig.3.

	x_1x_2			
	00	01	11	10
00	00	00	11	01
01	11	01	10	01
11	00	00	10	10
10	11	10	11	10

Y_1Y_2

Fig.3

Find all the race conditions in the table; are the races critical or noncritical? And do any cycles exist in the table?

7

- a) Derive the homing sequence for the sequential circuit defined by the state table in fig.4

	x	
	0	1
A	C/0	A/1
B	A/1	B/0
C	D/0	B/1
D	B/1	D/0

Fig.4

- b) Draw an ASM chart and state table for a 2-bit up-down counter having mode control input $M=1$ for down and $M=0$ for up counting