

2124  
B.E. (Electrical and Electronics Engineering)  
Third Semester  
PC-EE-303: Analog Electronics

Time allowed: 3 Hours

Max. Marks: 50

**NOTE:** Attempt five questions in all, including Question No. I which is compulsory and selecting two questions from each Unit.

x-x-x

I. Attempt the following:-

- a) Why common collector is called as emitter follower. Give reasons.
- b) Design a positive clipper circuit.
- c) In CB, current amplification is 0.9. If emitter current is 1mA, calculate base current.
- d) Plot the transfer characteristics of a depletion type JFET.
- e) If two inputs to a differential amplifier is 150 and 140 $\mu$ V, calculate output voltage if gain is 2000.

(5x2)

**UNIT - I**

- II. a) Find the transistor currents if it has  $\beta=100$ ,  $R_c=3K\Omega$ ,  $R_B=200K\Omega$ ,  $V_{BE}=5V$  and  $V_{CB}=10V$ ,  $I_B=2\mu A$   
b) Draw and explain the circuit to minimize thermal run away in transistors. (2x5)
- III. Determine the Q-point in a fixed bias circuit when a dc supply of 12V is applied to the transistor of gain 200. If the base resistance and collector resistance is 200K $\Omega$  and 200 $\Omega$  respectively, justify the location of operating point in the characteristic. (10)
- IV. Plot and explain the drain and transfer characteristics of P type MOSFET for both depletion and enhancement mode. (10)

**UNIT - II**


- V. If the input to a circuit is a sine waveform and its output is a square waveform, then determine the circuit used to realise this using operational amplifier. Explain the working of circuit using suitable mathematical relation. (10)

P.T.O.



(2)

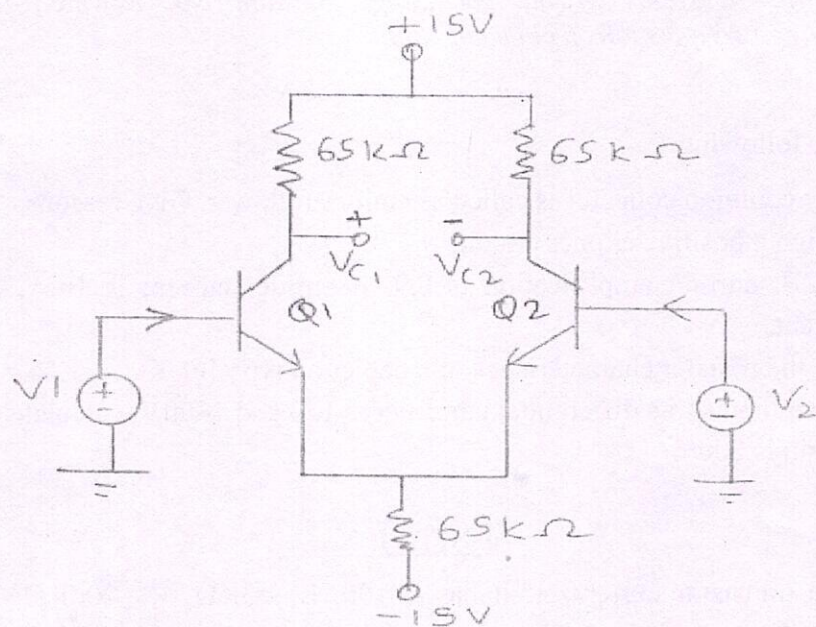- VI. In the differential amplifier circuit shown below, the transistors have identical characteristics and their  $\beta = 99$ . Determine the (i) Quiescent point (ii) configuration used. Assume  $V_{be} = 0.7V$ .



(10)

- VII. Describe any two of the following Op-Amp based circuit:

- Precision Rectifier
- Zero crossing Detector
- Any A/D converter

(2x5)

x-x-x