

2124
B.E. (Electrical and Electronics Engineering)
Third Semester
EE-307: Analog and Digital Electronics

Time allowed: 3 Hours

Max. Marks: 50

NOTE: Attempt five questions in all, including Question No. 1 which is compulsory and selecting two questions from each Section.


x-x-x

1. (a) Briefly describe the parameters affecting the bias stabilization of a transistor.
(b) Describe slew-rate of an op-amp.
(c) Convert the following to other canonical form: $F(x, y, z) = \sum(1,3,5,7)$.
(d) Differentiate edge triggering and level triggering.
(e) Find the 10's complement of $(935)_{11}$.

(5×2)

Section-A

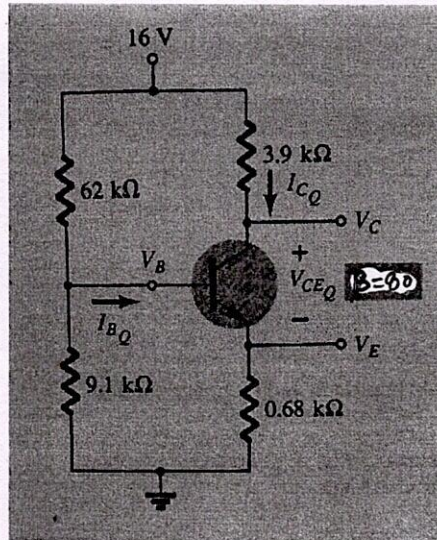2. (a) For the voltage-divider bias configuration shown in figure, determine I_{BQ} , I_{CQ} , V_{CEQ} , V_C , V_E , V_B .
(5)



- (b) Given $I_E(dc) = 1.2mA$, $\beta = 120$, $r_o = 40k\Omega$, sketch the common-emitter hybrid equivalent model. (5)
3. (a) Calculate the gain, input, and output impedances of a voltage-series feedback amplifier having $A = -300$, $R_i = 1.5k\Omega$, $R_o = 50k\Omega$, and $\beta = -1/15$. (5)

P.T.O.

(2)

- (b) Describe the working of a phase-shift oscillator. What are the conditions for a feedback circuit to be used as an oscillator? (5)
4. (a) Describe the differential and common-mode operation of an op-amp. Calculate the CMRR (in dB) for the circuit with $V_d = 1 \text{ mV}$, $V_o = 120 \text{ mV}$, and $V_c = 1 \text{ mV}$. Make any required assumptions. (5)
- (b) Describe the application of op-amp as a low-pass active filter. (5)

Section-B

5. (a) Simplify the Boolean expression and implement SOP form for (5)

$$F(A, B, C, D) = \sum m(0, 3, 4, 6, 7, 9, 11, 13)$$

- (b) Implement the function using a 8×1 multiplexer and external gates (5)

$$F(A, B, C, D) = \sum m(1, 2, 3, 7, 10, 11, 12)$$

6. (a) Describe the working of a master-slave flip-flop. How does it avoid race-around condition? (5)
- (b) Design a 3-bit synchronous counter going through the states: 1, 2, 6, 7. (5)
7. (a) Describe the working of counter-ramp type analog to digital converter with the help of a block diagram. Determine the resolution of a 10-bit A/D converter having a full scale analog input voltage of 5 V. (5)
- (b) Describe the working of a sample and hold switch. (5)

x-x-x