

Exam.Code:0941
Sub. Code: 33866

2124
B.E. (Mechanical Engineering)
Fifth Semester
MEC-505: Mechatronics

Time allowed: 3 Hours

Max. Marks: 50

NOTE: Attempt five questions in all, including Question No. 1 which is compulsory and selecting two questions from each Part.

x-x-x

Question 1:

- (a) Why is impedance matching important in electrical circuits? Explain one practical scenario where impedance matching is critical.
- (b) Why is the common emitter configuration widely used in amplifiers compared to the common base or common collector configurations? Discuss its advantages in terms of gain and input/output impedance.
- (c) Why are semiconductor materials like silicon and germanium preferred over conductors or insulators for making electronic devices? Discuss the role of the bandgap in determining their suitability.
- (d) Why would an inverting amplifier configuration be preferred over a non-inverting configuration in certain applications? Discuss its advantages in terms of gain control and phase inversion.
- (e) Why are sample-and-hold circuits critical in analog-to-digital conversion? Explain their role in preserving signal accuracy during the conversion process.

[10 marks]

Part A

Question 2. A circuit consists of the following:

A 12 V voltage source connected in series with a $4\ \Omega$ resistor (R_1) and a $2\ \Omega$ resistor (R_2). Parallel to R_2 is another branch containing a $6\ \Omega$ resistor (R_3).

- a. Determine the Thevenin equivalent voltage and resistance across the terminals of R_3 .
- b. Replace R_3 with a load resistor R_L . Derive the value of R_L that will maximize the power delivered to it (impedance matching principle).
- c. Calculate the maximum power delivered to R_L .

[10 marks]

Question 3:

- a. Explain the working principle of a Zener diode in reverse bias and its role in voltage regulation.
- b. Design a simple voltage regulator circuit using a Zener diode for an input voltage range of 12–18 V to provide a constant 9 V output. Explain the working of your design, and discuss the limitations of using a Zener diode for regulation in high-current applications.
- c. Compare the behavior and applications of optoelectronic diodes (LEDs and photodiodes) in electronic circuits.

[10 marks]

P.T.O.

(2)

Question 4:

- a. Explain the working principles of an inverting amplifier and a non-inverting amplifier using an operational amplifier. Derive expressions for their respective voltage gains.
- b. Discuss how the limitations of a real operational amplifier (e.g., finite gain, input bias current, offset voltage) impact the performance of the designed circuit.

[10 marks]

Part B**Question 5:**

- a. Explain the steps involved in deriving a simplified Boolean expression from a given truth table. Discuss how Karnaugh Maps (K-maps) help in minimizing Boolean expressions compared to algebraic simplification.
- b. Design a combinational logic circuit that takes three inputs (A,B,C) and outputs 1 only when a majority of the inputs are 1. Provide the truth table, simplified Boolean expression, and a block diagram for your design.
- c. Discuss the advantages and limitations of using NAND gates to implement any digital logic function.

[10 marks]

Question 6:

- a. Discuss the working principles and structure of a Programmable Logic Controller (PLC). How does it differ from a traditional microcontroller?
- b. Write and explain a ladder logic program to control a conveyor belt system where: The conveyor starts when a start button is pressed. It stops when a stop button is pressed or a proximity sensor detects an object. Include an emergency stop that overrides all other conditions.
- c. Explain how a shift register can be implemented in ladder programming and its applications in industrial automation.

[10 marks]

Question 7:

- a. Explain the working principles of cams and followers, and discuss their applications in mechanical systems. Illustrate your explanation with a diagram of a cam profile for uniform motion.
- b. Compare and contrast belt drives and chain drives in terms of efficiency, maintenance, and applications in mechatronic systems.
- c. Using an example, describe how kinematic chains are used to achieve complex motion in mechatronic systems, such as robotic arms or assembly line equipment.

[10 marks]