

2014
B.E. (Computer Science and Engineering)
Second Semester
CS-203: Digital Electronics and Logic Design

Time allowed: 3 Hours

Max. Marks: 50

NOTE: Attempt five questions in all, including Question No. I which is compulsory and selecting two questions from each Section.

x-x-x

I	a	Differentiate between multiplexer and demultiplexer.	
	b	What are the applications of 'D' flip-flop?	
	c	List the characteristics of standard TTL and open collector TTL	
	d	Give difference between Synchronous and Asynchronous counters.	
	e	What are the applications of shift registers?	(5 X 2 =10)
Section A			
II	a	Design and explain BCD to 7-segment decoder.	(5)
	b	What is carry look-ahead adder? Explain with the help of suitable circuit diagram.	(5)
III	a	Simplify the Boolean expression using K-MAP $Y(A, B, C, D) = \sum m(1, 2, 3, 8, 9, 10, 11, 14) + d(7, 15)$	(5)
	b	What are universal gates? Implement XOR and OR gates using minimum number of NAND gates only?	(5)
IV	a	Explain parity generator and checker with circuit diagram.	(5)
	b	Explain conversion of Gray to Binary. Design 3 bit Gray to Binary code converter with the help of suitable circuit diagram.	(5)
Section B			
V	a	Design Full adder circuit using 4:1 multiplexer (two in number only).	(5)
	b	Design synchronous counter using T flip-flop to count the following sequence 0,5,6,3,7,4,1	

(2)

		Avoid lockout condition.	(5)
VI	a	Explain J-K flip flop. Why master slave flip flop is used?	(5)
	b	What do you mean by counters. Implement 3 bit up-down asynchronous counter.	(5)
VII		Write a short note on:	
	a	FPGA and its applications.	(5)
	b	State Reduction and State Assignment.	(5)

x-x-x