

2014
B.E. (Electronics and Communication Engineering)
Second Semester
EC-203: Digital Design

Time allowed: 3 Hours

Max. Marks: 50

NOTE: Attempt five questions in all, including Question No. 1. (Section-A) which is compulsory and selecting two questions each from Section B-C.

x-x-x

Section A		
1	<ul style="list-style-type: none"> i. What is universal gate? Realize OR gate using universal gates. ii. Differentiate minterm and maxterms in a Boolean expression. iii. What is an inhibited state and when occurs in a flip-flop? iv. Which one is the fastest A/D converter and why? v. Which one is the fastest bipolar logic family and why? 	10
Section B		
2	<ul style="list-style-type: none"> a) Minimize and design the function $\sum m(0,1,6,7,8,9,13,14,15)$ using only minimum number of NAND gate if complementary inputs are also available. b) What is race around condition in a flip-flop? How it can be avoided? 	5 5
3	<ul style="list-style-type: none"> a) Implement a full adder with decoder and gates. b) Design a four bit magnitude comparator. 	5 5
4	<ul style="list-style-type: none"> a) Convert T to D and J-K to S-R flip-flops. b) List the PAL programming table for BCD to excess-3 code converter. 	5 5
Section C		
5	<ul style="list-style-type: none"> a) Design a 3-bit synchronous counter to count sequence 0,2,4,5,7 and repeat using J-K flip-flop. b) What is bidirectional shift register? Draw and explain a 4-bit bidirectional shift register. 	5 5
6	<ul style="list-style-type: none"> a) What are the drawbacks of weighted-resistor D/A converter? How these drawbacks can be overcome using R-2R ladder type D/A converter? b) Draw and explain 2-input CMOS NAND and NOR gates. 	5 5
7	<ul style="list-style-type: none"> a) Explain construction and working of TSL inverter. b) Differentiate a ring counter and twisted ring counter. Explain working of 4-bit Johnson's counter. 	5 5

x-x-x