

2014

B.E. (Electrical and Electronics Engineering)

Sixth Semester

EE-611: Programmable Logic Controller and Distributed Control System

Time allowed: 3 Hours

Max. Marks: 50

*NOTE: Attempt five questions in all, including Question No. 1 which is compulsory and selecting two questions from each section. All questions carry equal marks.*

x-x-x

1)

- a) What is sourcing and sinking in PLC.
- b) State two ways in which I/O is incorporated into the PLC.
- c) List different network topology used for DCS.
- d) Define Scan type of PLC.
- e) Explain the differences between open and proprietary PLC architecture.

**Section A**

2)

- a) Explain in detail the factors responsible for difficulties encountered in implementation of process control.
- b) Compare the PLC and PC with regard to:
  - a. Physical hardware differences
  - b. Operating environment
  - c. Method of programming
  - d. Execution of program

3)

- a) Compare discrete and analog I/O modules with respect to the type of input or output devices with which they can be used.
- b) Discuss Discrete AC input module with suitable diagrams.

4)

- a) Draw and explain the connection diagram and ladder program for a motor control in forward and reverse direction with interlocking.
- b) Answer the following with regard to a ladder logic rung:
  - a. Describe the basic makeup of a ladder logic rung.
  - b. How are the contacts and coil of a rung identified?
  - c. When is the ladder rung considered as having logic continuity?.

P.T.O.



(2)

Section - B

5)

- a) Draw and explain the hierarchy of DCS.
- b) Draw and explain the ladder logic for program that uses a TON timer to illuminate a green pilot light for 20 seconds each time a momentary button is pressed.

6)

- a) Construct a ladder diagram for traffic lights control with following sequence:  
The timed sequence of the lights is:
  - Red—30 s on
  - Green—25 s on
  - Amber—5 s on
  - The sequence then repeats itself.
- b) There are three machines, each with its own start stop buttons. Only one may run at a time. Construct a ladder diagram with appropriate interlocking.

7)

- a) Explain a TOF delay timer.
- b) Differentiate between data logging and data acquisition.