

2014
B.E. (Electrical and Electronics Engineering)
Sixth Semester
PE-EE-603: Programmable Logic Controllers

Time allowed: 3 Hours

Max. Marks: 50

NOTE: Attempt five questions in all, including Question No. 1 which is compulsory and selecting two questions from each Unit.

x-x-x

I. Answer the following:-

- a) Draw a schematic of input modules of PLC?
- b) How JUMP differs from SKIP and MCR functions.
- c) List the examples of counter functions.
- d) State any two features of DCS.
- e) State I/O list for bottle filling application.

(5x2)

UNIT - I

- II. Explain, in detail, the internal structure of PLC. Discuss about the programming formats of PLC. Write the advantages and disadvantages of PLC (two each). (10)
- III. What is a ladder diagram? Explain the ladder diagram and the sequence signals of a 4-bit shift register. (10)
- IV. a) Draw equivalent ladder diagram for the instruction shown below:
LD X400
OR X402
LD X401
OR X403
AND
OUT X430
END
b) Explain NOT gate and relay and PLC equivalents. (6,4)

P.T.O.

(2)

UNIT - II

- V. a) Explain different types of timers with timing diagrams.
b) Draw a PLC wiring diagram for control of a lamp from two switches. (6,4)
- VI. Develop a generalized DCS architecture for control of a plant. Explain each level in detail. (10)
- VII. Write short notes on:
a) SCADA
b) Retentive timer (2x5)

x-x-x