

2074

B.E. (Electrical and Electronics Engineering)
Third Semester
PC-EE-303: Analog Electronics

Time allowed: 3 Hours

Max. Marks: 50

NOTE: Attempt five questions in all, including Question No. I which is compulsory and selecting two questions from each Section.

X-X-X

I.

- a) What is the difference between Avalanche breakdown and Zener breakdown?
- b) Find output resistance of BJT for early voltage of 100 V and collector current of 1mA.
- c) Draw I_D - V_{DS} characteristics of MOSFET.
- d) Define slew rate. How it affects Op-Amp performance?
- e) Which type of feedback is applied to the oscillators?

[5×2=10]

SECTION A

- II. a) Give small signal model of diode and derive expression for its dynamic resistance. [5]
b) A silicon diode has a reverse saturation current of 0.20 pA at 30°C. Find the diode current when it is forward biased by 0.65V at a temperature of 100°C. [5]
- III. a) Consider a common emitter circuit using a BJT having $I_S = 10^{-15}$ A, a collector resistance $R_C = 6.8$ k Ω and a power supply = 10V. Determine the value of bias voltage V_{BE} required to operate the transistor at $V_{CE} = 3.2$ V. What is the corresponding value of collector current I_C ? [5]
b) With the help of suitable diagrams, explain how BJT is used as an amplifier and as a switch. Draw transfer characteristics for CE configuration. [5]
- IV. a) Draw device structure and explain physical operation of MOSFET in enhancement mode with and without gate voltage. [5]
b) For a MOSFET with $W/L = 8\mu\text{m}/0.8\mu\text{m}$, calculate values of V_{GS} and V_{DSmin} needed to operate it in the saturation region with a dc current $I_D = 100$ μ A. [5]

SECTION B

- V. a) Draw and explain equivalent circuit of an opamp. Plot its ideal voltage transfer curve. [4]
b) Define the terms: CMRR, Output offset voltage and Gain bandwidth product. [6]
- VI. a) With the help of suitable diagram, explain functioning of integrator and derive expression for its output voltage. Plot frequency response of basic and practical integrator? [5]
b) Design a Phase Shift oscillator using op-amp for output frequency of 1 kHz. [5]
- VII. Write note on following:
a) Instrumentation Amplifier [5]
b) Peak detector [5]

X-X-X