

2074  
B.E. (Electrical and Electronics Engineering)  
Seventh Semester  
EE-710: Power Electronic and Drives

Time allowed: 3 Hours

Max. Marks: 50

NOTE: Attempt five questions in all, including Question No. 1 which is compulsory and selecting two questions from each Part. Assume suitably missing data, if any.

x-x-x

x-x-x

1. a.	Name the practical gating signal for an AC voltage controller. Also give its advantages.	(2)
b.	Write the expressions of output voltage, $v_o$ for a complete cycle for a half-bridge inverter.	(2)
c.	Write the electro-dynamic equation of a drive system in differential form.	(2)
d.	Write the relationship between output frequency, input frequency and reduction factor for a three-phase to single-phase cycloconverter.	(2)
e.	By which method the torque can be kept maximum in all the speed range of induction machine drive system?	(2)

Part-A

2. a. Draw the output voltage and current wave-shapes for single-phase full-wave AC voltage controller feeding a resistive load. (4)
- b. A single-phase full-wave ac voltage controller feeds a resistive load of  $R=20$  ohms with an input voltage of 230 V, 50 Hz. Firing angle for both the thyristors is 45 degrees. Find (2,4)
- (a) rms value of output voltage
  - (b) load power and input power-factor.
3. A three-phase bridge inverter delivers power to a resistive load from a 450 V dc source. For a star-connected load of 10 ohms/phase, determine (5,5)
- (a) rms value of load current
  - (b) rms value of thyristor current
- for 180 degree mode operation of this inverter.
4. Explain the operating principles of:
- a. Single-phase half-bridge inverter. (5)
  - b. Single-phase half-wave ac voltage controller. (5)

P.T.O.



(2)

**Part-B**

5. Explain the working of single-phase to single-phase circuit step-down cycloconverter with discontinuous load current. (10)
6. a. Explain the working of 3-phase full-converter feeding a separately excited dc motor with voltage,  $v_t$  and current waveforms,  $i_a$ ,  $i_A$  and  $i_{T1}$  for firing angle of 30 degrees. (8)
- b. Also, write the expression for average output terminal voltage,  $v_t$  of the armature circuit. (2)
7. Write short notes on the following:
- a. Stator voltage control of Induction motor drive system. (5)
- b. Operation of two-quadrant chopper drive. (5)

x-x-x