

Exam.Code:0970
Sub. Code: 7054

2054
M.E. (Electronics and Communication Engineering)
Second Semester
ECE-1205: VLSI Design

Time allowed: 3 Hours

Max. Marks: 50

NOTE: Attempt five questions in all, including Question No. 1 which is compulsory and selecting two questions from each Unit.

x-x-x

I. Answer the following:-

- a) What is a pass transistor? How it is different to a MOS inverter?
- b) Explain two short channel effects in a MOSFET.
- c) Differentiate between local routing and global routing.
- d) Explain the working of a RS flipflop.
- e) What are ratioed circuits? Give examples

(5x2)

UNIT - I

- II. a) Differentiate between accumulation, inversion and depletion regions of a MOSFET.
b) Explain why drain ON current does not increase in saturation region. (5,5)

- III. a) Differentiate between a CMOS inverter and a MOS inverter with active load.
b) What is an active resistor?
c) What is a basic difference between an NMOS pass transistor and a CMOS transmission gate? (3,3,4)

IV. Write notes on:-

- a) CMOS NOR gate working
- b) CMOS half adder.

(5,5)

UNIT - II

- V. a) Explain how a VLSI digital circuit can be described using a language? Explain the salient features and types of such a language.
b) Differentiate between full custom VLSI design and a semi custom VLSI design.

(5,5)

P.T.O.

(2)

- VI. a) Explain and compare the terms placement and floor planning. What are their types?
Name two of the algorithms of placement and floor planning.
- b) Explain how the clock is distributed in a VLSI chip? (7,3)

VII. Write notes on:-

- a) Power line distribution in a VLSI layout
- b) Types of routing in a VLSI layout. (5,5)

x-x-x