

20619
M.E. Electrical Engineering (Power System)
Second Semester
EE-8204(b): Power Electronics Converters for Smart Grid

Time allowed: 3 Hours

Max. Marks: 50

NOTE: Attempt any five questions.

x-x-x

1. Derive the expression for duty cycle 'D' of a buck-boost converter with suitable waveforms under continuous and discontinuous conduction mode. (10)
2. a) In a step-up converter, consider all components to be ideal. Let V_d be 8-16V, $V_o = 24V$ (regulated), $f_s = 20$ kHz and $C = 470 \mu F$. Calculate L_{min} that will keep the converter operating in a continuous -conduction mode if $P_o \geq 5W$.
b) Explain the operating principle of parallel loaded resonant dc-dc converter under discontinuous conduction mode with suitable diagrams. (3,7)
3. Explain the Uni-polar, bi-polar and isolated drive configurations with suitable diagram. (10)
4. Discuss the sine wave PWM and space vector modulation (SVM) strategies, and compare them in terms of total harmonic distortion (THD), switching losses, and output voltage waveform quality. (10)
5. In a single-phase full-bridge PWM inverter, the input DC voltage varies in a range of 295-325 V Because of the low distortion required in the output v_o , $m_a \leq 1.0$.
(a) What is the highest V_{o1} , that can be obtained and stamped on its voltage rating?
(b) Its nameplate volt-ampere rating is specified as 2000VA, that is, $V_{o1,max} I_{o,max} = 2000$ VA, where i_o is assumed to be sinusoidal. Calculate the combined switch utilization ratio when the inverter is supplying its rated volt-amperes. (10)
6. Describe the topology of cascaded multi-level inverters (MLIs) commonly employed in grid-tied photovoltaic (PV) systems. Explore techniques for reducing harmonic distortion in an MLI for enhancing power quality. (10)

P.T.O.

(2)

7. Consider the step-down converter circuit shown in Fig. 1 without the turn-on snubber. The dc input voltage V_d is 500V, the load current $I_o=500A$, and the switching frequency is 1 kHz. The free-wheeling diode has a reverse-recovery time $t_{rr} = 10\mu s$. The GTO has a current fall time $t_{ff}=1\mu s$, a maximum reapplied voltage rate $dv/dt = 50 V/\mu s$, and a maximum controllable anode current $I_{AM}=1000A$.

- (a) Find the appropriate values for resistance R_s and capacitance C_s for the turn-off snubber circuit.
 (b) Estimate the power dissipated in the snubber resistance.

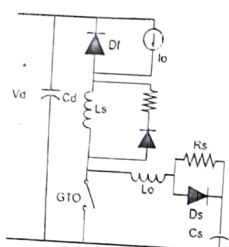


Fig. 1

8. (a) The turn-off snubber for a thyristor does not include a diode as it does for the BJT and MOSFET. Explain Why? (10)
 (b) Explain the effect of adding a snubber resistance with suitable waveforms. (2x5)

x-x-x