

Exam.Code:0976

Sub. Code: 7114

2054

M. Tech. (Microelectronics)

Second Semester

MIC-203: Analog and Mixed Signal Device Design

Time allowed: 3 Hours

Max. Marks: 50

*NOTE: Attempt five questions in all, including Question No. 1 which is compulsory and selecting two questions from each Unit.*

*x-x-x*

I. Attempt the following:-

- a) Write a short note on successive approximation multiplier with block diagram.
- b) Explain about CMOS sample and Hold circuit.
- c) Explain the working simple MOS current mirror.
- d) What is slew rate and derive the linear settling response.
- e) What is common mode response and CM gain with its significance? (5x2)

**UNIT - I**

- II. What is an analog multiplier? Explain the concept of 2-quadrant analog multiplier. Discuss the significance of Gilbert Cell over 2-quadrant multiplier and its applications. (10)
- III. a) Derive and explain the small signal gain of source follower.  
b) Calculate the small signal output resistance and Body effects included in source follower. (2x5)
- IV. Evaluate the voltage gain of a MOSFET based two input differential amplifier. Differentiate between a MOS based and bipolar based differential amplifiers. (10)

**UNIT - II**

- V. What is need of compensation in op-amp amplifiers? Describe any two techniques used for compensation in two stage op-amp amplifiers. (10)
- VI. What are Widlar and Wilson current sources? Explain their working and temperature dependence. (10)

P.T.O.

(2)

- VII. a) Design a circuit to obtain a current  $I_D$  of  $80 \mu\text{A}$  in fig 1. Find the value required for  $R$  and find the DC voltage  $V_D$ . NMOS transistor has  $V_t=0.6\text{V}$ ,  $\mu_n C_{ox}=200\mu\text{A}/\text{V}^2$ ,  $L=0.8\mu\text{m}$  and  $W=4\mu\text{m}$  (Assume  $\lambda=0$ ).

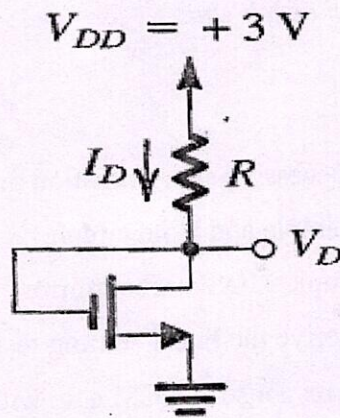


Fig 1

- b) Derive the integral and differential non-linearity of the voltage scaling DAC. Also, illustrate the application with an example. (2x5)

x-x-x