

2125
M. Tech. (Micro-Electronics)
First Semester
MIC-103: MOS Integrated Circuit Modeling

Time allowed: 3 Hours

Max. Marks: 50

NOTE: Attempt five questions in all, including Question No. 1 which is compulsory and selecting two questions from each Unit.

x-x-x

I. Answer the following:-

- a) What is MOSFET modeling? What are model parameters? Differentiate between charge based and voltage-based MOS modeling.
- b) Differentiate between NMOS pass transistor and a CMOS transmission gate.
- c) What is the role of a clock in a digital logic? Give one example.
- d) What is the difference between a random logic and a structured logic?
- e) Give two advantages of a BiCMOS inverter as compared to a CMOS inverter. (5x2)

UNIT - I

- II. a) Explain how inversion takes place in a MOSFET? Explain how MOS capacitance varies with the applied gate voltage?
- b) List two short channel effects arising in the deep sub micron MOSFETs. And explain why these effects are not desirable. (5,5)

- III. a) What is an active resistor? Give its working. How it is different to a passive resistor?
- b) Compare the working of a CMOS inverter and a NMOS inverter with active load. (4,6)

IV. Write notes on:-

- a) Gate delay and interconnection delays in digital circuits.
- b) Dynamic power dissipation in CMOS circuits (5,5)

UNIT - II

- V. a) Differentiate between PMOS pass transistors and CMOS transmission gate used in the digital logic and compare the delays in both logics.
- b) What is a depletion load MOSFET? How it is different to the enhancement load MOSFET? (5,5)

P.T.O.

(2)

VI. a) Explain using a neat diagram the working of a CMOS based SR latch.

b) What is the role of a clock in sequential circuits?

(5,5)

VII. Write notes on :-

a) Depletion mode MOSFET

b) Dynamic CMOS circuits.

(5,5)

x-x-x