

2125
B.E. (Electrical and Electronics Engineering)
Third Semester
PC-EE-4303: Analog Electronics

Time allowed: 3 Hours

Max. Marks: 50

NOTE: Attempt five questions in all, including Question No. 1 which is compulsory and selecting two questions from each Unit.

x-x-x

I. Answer the following:-

- a) A silicon diode with forward drop $V_D=0.7\text{ V}$ is connected in series with a $1\text{ k}\Omega$ resistor to a 12 V battery. Find the diode current I_D .
- b) Why is the full-wave rectifier preferred over the half-wave type?
- c) How does temperature affect MOSFET characteristics?
- d) State the barkhausen criteria for oscillations?
- e) What are the ideal characteristics of op-amp? (5x2)

UNIT - I

- II. What is a clipping circuit? Explain its working with waveforms as positive clippers and negative clippers. (10)
- III. a) Determine the Q-point in a fixed bias circuit when a dc supply of 12V is applied to the transistor of gain 200. If the base resistance and collector resistance is $200\text{K}\Omega$ and 200Ω respectively, justify the location of operating point in the characteristic.
- b) Show that the Q-point in voltage divider biasing circuit is independent of the current gain. (10)
- IV. Describe the construction of an p-channel enhancement MOSFET with a neat diagram. For a MOSFET amplifier with load $R_D=10\text{ k}\Omega$ and $g_m=2\text{ mS}$, find voltage gain A_v ? (10)

UNIT - II

- V. Draw the block diagram of op-amp and analyse its performance as a differentiator. (10)

P.T.O.

(2)

- VI. a) Determine the output voltage for inverting amplifier if (a) $V_{in}=20\text{mV}$ dc.
b) (i) $V_{in}=-50\ \mu\text{V}$ peak sine wave. Assume op-amp is 741.
(ii) Define the following electrical parameters : input offset voltage, input resistance, CMRR, output voltage swing and slew rate. (10)
- VII. Draw the schematic for a hysteric comparator and explain its operation for different reference voltages. Also assume reference to be 0V and then again plot its output waveforms. (10)

x-x-x