

Exam.Code:0929

Sub. Code: 33668

2125

B.E. (Electronics and Communication Engineering)

Fifth Semester

EC-505: Digital System Design

Time allowed: 3 Hours

Max. Marks: 50

NOTE: Attempt five questions in all, including Question No. 1 which is compulsory and selecting two questions from each Part.

x-x-x

[5X2=10]

1. (a) Simplify the Boolean expression using Boolean laws: $AB+A'B+AB'$
 - (b) Explain the term "hazard" in digital system design.
 - (c) What is the difference between simplification and minimization of Boolean functions?
 - (d) Differentiate between single error detection and single error correction.
 - (e) Why is the K-map method preferred over the Boolean algebra method for minimization?.

Part-A

2. (a) What is the tabular method for minimization, and when is it preferred over the K-map method? [5]
 - (b) Explain switching algebra and state its importance in digital system design. [5]
3. (a) Describe any two methods used for detecting and locating faults in combinational circuits. [5]
 - (b) What is the iterative consensus method in Boolean function minimization? [5]
4. What are the techniques to minimize propagation and wire delays in digital system design? Explain with examples. [10]

Part-B

5. (a) Draw the truth table of a JK flip-flop and explain how it can be used to eliminate the "race around" problem. [5]
 - (b) Compare synchronous and asynchronous counters in terms of speed and design complexity. [5]
6. Design a sequence detector that outputs 1 whenever the input sequence 101 appears in a serial input stream. Draw the state diagram and provide the excitation table for implementation with D flip-flops. [10]
7. Write a note on:
 - (a) Synthesis using sequential machines. [5]
 - (b) Fault Detection and Correction. [5]

x-x-x