

Exam.Code:0906  
Sub. Code: 33267

2015  
B.E., Second Semester  
EEEC-X01: Basic Electrical and Electronics Engineering

Time allowed: 3 Hours

Max. Marks: 50

**NOTE:** Attempt five questions in all, including Question No. 1 which is compulsory and selecting two questions from each Unit.

X-X-X


I. Attempt the following:-

- State and prove maximum power transfer theorem.
- Describe a star and delta connected system.
- What do you mean by losses and efficiency of a transformer?
- Draw the circuit diagram of DCTL to perform logical AND.
- What are the advantages of FET over BJT?

(5x2)

UNIT - I

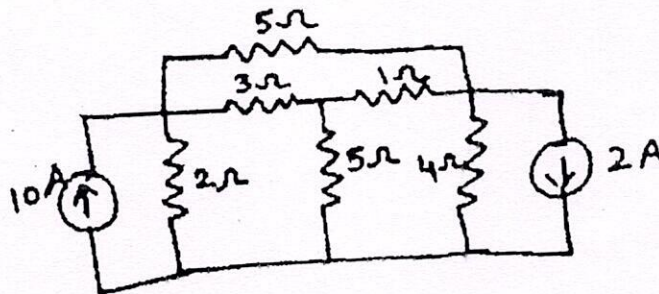II. Use nodal analysis to find the currents in various resistors of the circuit shown in this figure.



(10)

- III. a) Two impedances  $z_1 = 10 + j5\Omega$  and  $z_2 = 8 + j6\Omega$  are connected in parallel across a voltage  $V = 200 + j0$ . Calculate the circuit current, power factor and reactive power.
- b) Show how three-wattmeter method can be used for power measurement with the help of diagram.

(2x5)

P.T.O.



(2)

- IV. What do you mean by open-circuit and short-circuit test on transformers? Obtain the equivalent circuit of 1- $\phi$ , 4kVA, 200/400 V, 50 Hz transformer from following test results:

O.C.  $\rightarrow$  200V, 0.7A, 70W (L.V. primary side)

S.C.  $\rightarrow$  15V, 10A, 80W (H.V. Secondary side) (10)

UNIT - II

- V. a) What is zener diode? Explain its use as voltage regulator.  
b) Why NAND gate is called a universal gate? Explain with examples. (2x5)
- VI. a) Draw the logic circuit for  
$$Y = A\bar{B}C + ABC$$
  
and then simplify and draw simplified circuit.  
b) Draw the basic characteristics of a BJT. Discuss its operation in common base mode. (2x5)
- VII. Write notes on the following:-  
a) Clipper and clampers  
b) Light Emitting diode (2x5)

x-x-x