

Exam.Code:0906  
Sub. Code: 33306

2015  
B.E. (Electrical and Electronics Engineering)  
Second Semester  
EEEC-201: Basic Electrical Engineering

Time allowed: 3 Hours

Max. Marks: 50

*NOTE: Attempt five questions in all, including Question No. 1 which is compulsory and selecting two questions from each Unit.*

x-x-x

I. Answer the following:-

- a) Give the relation between phase and line values of voltage and current for star connection.
- b) What is the working principle of d.c. motor?
- c) Explain the working principle of Norton theorem.
- d) What are the different types of losses in a transformers?
- e) Draw single line diagram of distribution network. (5x2)

**UNIT - I**

- II. a) With respect to D.C. circuit, state and explain Kirchhoff's law.  
b) A sinusoidally varying alternating voltage is given by  $v(t) = V_m \sin \omega t$ , obtain its RMS value of voltage in terms of maximum value. (2x5)
- III. What currents flow in a single-phase star connected motor? Draw its circuit diagram with its phasor representation? What is power factor in RLC series circuit at leading, lagging and resonance conditions? (10)
- IV. Show that two Wattmeters are sufficient to measure three-phase power. Three similar coils each having  $R = 10\Omega$ , and  $X = 8\Omega$  are connected in star across 400V, 3-phase supply. Determine line current, total power and reading of each wattmeter connected to measure power. (10)

P.T.O.



(2)

**UNIT - II**

- V. Give the classification of transformers on the basis of voltage ratio, construction and application. Derive the emf equation of a single-phase transformer from basic rules. (10)
- VI. a) A dc motor running at a speed of  $N$  rpm, obtain an expression for emf induced in the armature winding.  
b) With the help of neat diagram, explain the constructional details of three-phase induction motor. (2x5)
- VII. a) Prove that hysteresis loss in a magnetic material is equal to area of hysteresis loop.  
b) Define the terms mmf, magnetic flux and magnetic reluctance and establish the relation which holds between these quantities for a magnetic circuit. (2x5)

x-x-x