

2055

B.E., Second Semester  
EC-204: Electrical Science

Time allowed: 3 Hours

Max. Marks: 50

**NOTE:** Attempt five questions in all, including Question No. 1 which is compulsory and selecting two questions from each Section.

x-x-x

- I. Attempt the following:
- Define dependent and independent voltage and current source?
  - Define the principle behind superposition theorem.
  - Explain the concept of duality.
  - What is the composite filter?
  - Explain the role of concept of slip in electrical motors. (5x2)

### Section A

- II. a). Determine the current supplied by each battery in the circuit shown in fig. 1.

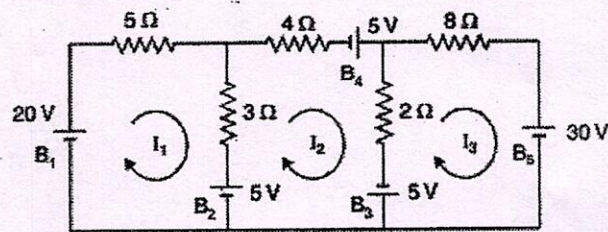


Fig. 1

- b). State and prove maximum power transfer theorem with example. (2x5)
- III. a). Find the Thevenin's equivalent of the circuit shown fig.2, across terminals a-b. Then find the current through  $R_L = 6$  ohms and 36 ohms respectively.

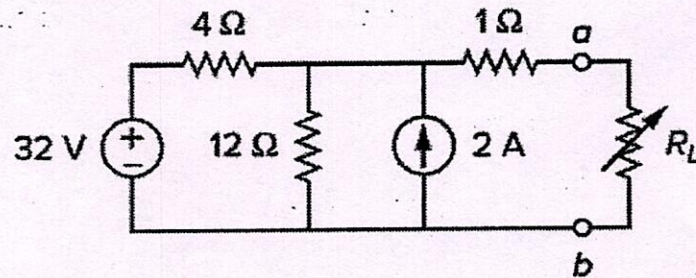


Fig. 2

- b). What is the relation between star and delta connections? (2x5)
- IV. a. Explain the concept of complex frequency. Also discuss its physical significance?
- b. Explain with reason, the given expression for the deriving point impedance is suitable or not for representing a passive network.

$$Z(s) = \frac{s^4 - s^3 + 2s^2}{(s+4)(s+3)} \quad (2x5)$$

P.T.O.



(2)

**Section B**

- V. Explain the following Two port network parameter.
- a). Short Circuit Impedance Parameters.
  - b). Hybrid Parameters. (2x5)
- VI. Design constant-k, m-derived filters and composite filter. (10)
- VII. a). Define the principle behind single phase induction motor. Write some applications.
- b). What are different speed control methods for DC motor. (2x5)

x-x-x