

2055
B.E., Second Semester
EEC-X01: Basic Electrical and Electronics Engineering
(Common with IT, CSE, MEC)

Time allowed: 3 Hours

Max. Marks: 50

NOTE: Attempt five questions in all, including Question No. 1 which is compulsory and selecting two questions from each Unit.


x-x-x

I. Attempt the following:-

- Explain the significance of power factor in an AC circuit.
 - Explain the working principle of p-n junction diode.
 - Why does saturation occur in a BJT and what are its implications?
 - Why do clamper circuit shift the DC level of a signal?
 - How the equivalent circuit helps in deciding the regulation of a transformers.
- (5x2)

UNIT - I

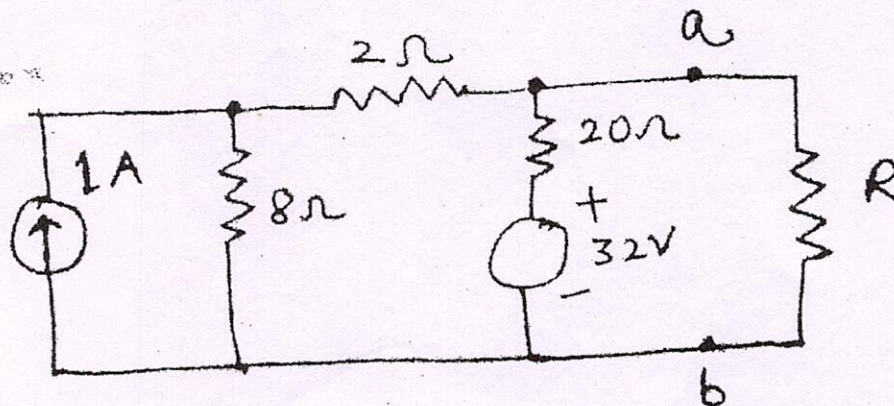- II. a) State and explain the maximum power transfer theorem. Derive the condition for maximum power transfer.
- b) Derive the expression for power in a balanced three-phase system. Explain the significance of real reactive and apparent power.
- (2x5)
- III. For the circuit shown in this figure, find the Thevenin voltage and Norton current using the principle of superposition.



(10)

P.T.O.

(2)

- IV. a) Derive the EMF equation of a transformer and explain each term involved.
b) A 100 KVA transformer has full load copper loss of 1.5KW and iron loss of 1.2 kW. Find the efficiency at full load and at 0.8 power factor lagging. (2x5)

UNIT - II

- V. a) Derive the working principle of a light emitting diode (LED). Explain how it differs from a normal diode.
b) A zener diode of 5V is used with a 12V supply and 220 Ω series resistor. Find the current through diode if load draws 20 mA. (2x5)
- VI. a) A transistor in CB configuration has $I_E = 1\text{mA}$, $I_C = 0.98\text{ mA}$. Find α and β
b) Explain the input and output characteristics of a transistor in common-base configuration. Discuss its applications. (2x5)
- VII. a) Discuss diode logic gates (AND, OR). Explain the circuit operation and limitations.
b) Explain the working of a half-wave and full-wave rectifier. Compare their performance parameters. (2x5)

x-x-x