

30/21

Exam.Code:0928  
Sub. Code: 33658

2055  
B.E. (Electronics and Communication Engineering)  
Fourth Semester  
EC-409: Network Analysis

Time allowed: 3 Hours

Max. Marks: 50

**NOTE:** Attempt five questions in all, including Question No. I which is compulsory and selecting two questions from each Unit. Missing data (If any) can be appropriately assumed.

x-x-x

**Q1 Explain briefly**

- A) State the Maximum power theorem for AC and DC circuit. (2)  
B) Obtain the lattice equivalent of a symmetric  $\Pi$ -network shown in Fig. 1 (2)

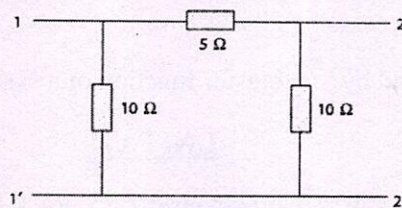


Fig.1

- C) Explain in following terms (i) Reflection factor (ii) Reflection loss (2)  
D) What are reciprocal and symmetrical networks? (2)  
E) Draw T-section and  $\Pi$ -section of a band-stop filter. (2)

**UNIT - I**

- Q2 A)** Determine the current  $i_1$  in the circuit of Fig. 2 using nodal analysis method and graph theory concepts. (5)

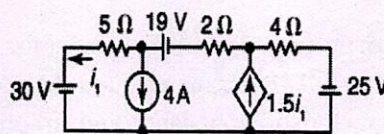


Fig.2

- B) Derive the expression used for the delta equivalent resistance from star connection. (5)  
**Q3 A)** Two identical sections of the circuit shown in fig. 3 are connected in series. Obtain the z-parameters of the combination and verify by direct calculation. (5)

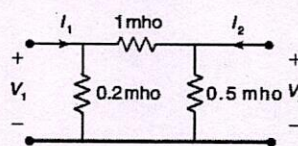


Fig. 3

Contd.....P/2



(2)

B) Find the h-parameters for the two-port network shown in Fig. 4. (5)

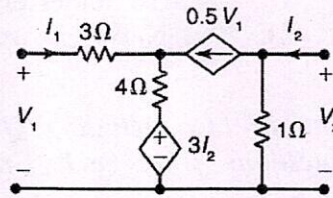


Fig.4

Q4 A) Draw poles and zeros for the transform voltage and evaluate  $V(t)$  either analytically or by making use of pole-zero diagram. (5)

$$V(s) = \frac{s^2 + 3s + 2}{s^2 + 7s + 12}$$

B) What do you understand by the transfer function of a system? State its properties. (5)

### UNIT - II

Q5 A) What are filters? Write and explain the properties of the filters. (5)

B) Write short notes on (5)

- (i) Butterworth filter
- (ii) all pass filter.

Q6 A) Design a band-elimination filter having a design impedance of  $600 \Omega$  and cut-off frequencies  $f_1 = 2 \text{ kHz}$  and  $f_2 = 6 \text{ kHz}$ . (5)

B) Define notch frequency. Explain the operational characteristics of an active notch filter. Where are these filters used? (5)

Q7 A) At  $8 \text{ MHz}$  the characteristic impedance of a transmission line as  $40 - j2 \Omega$  and the Propagation constant  $0.01 + j 0.18$  per meter. Find the primary constant. (5)

B) Explain in detail (i) Characteristic impedance and (ii) propagation constant (5)

x-x-x