

2055

B.E. (Electrical and Electronics Engineering)

Sixth Semester

PC-EE-601: Computer Aided Power System Analysis (CAPSA)

Time allowed: 3 Hours

Max. Marks: 50

NOTE: Attempt five questions in all, including Question No. 1 which is compulsory and selecting two questions from each Part.

x-x-x

1. (a) What are factors which affects steady state stability?
- (b) How transformer impedance on primary side is referred on secondary side in per unit.
- (c) Discuss role of secondary loop in LFC.
- (d) What are limitations of equal area criterion in transient stability analysis of multi-machine system?
- (e) What the role of ZBus in fault analysis?


(5*2=10)

PART-A

2. (a) The fuel cost function in Rs/ hr for two 800 MW thermal plants are given by:
 $C_1 = 400 + 6 P_1 + 0.04 P_1^2$
 $C_2 = 500 + \beta P_2 + \gamma P_2^2$
 where P_1 and P_2 are in MW.
 - (i) The increment cost of power λ is Rs 8/Mwh when the total power demand is 600 MW. Neglect losses, find optimal generation of each plant.
 - (ii) The increment cost of power λ is Rs 10/Mwh when the total power demand is 1500 MW. Neglect losses, find optimal generation of each plant.
 From the results of (i) and (ii), find fuel coefficients β and γ .
- (b) Discuss equal area criterion curves for sudden increase of power input to a synchronous machine.

(7,3)

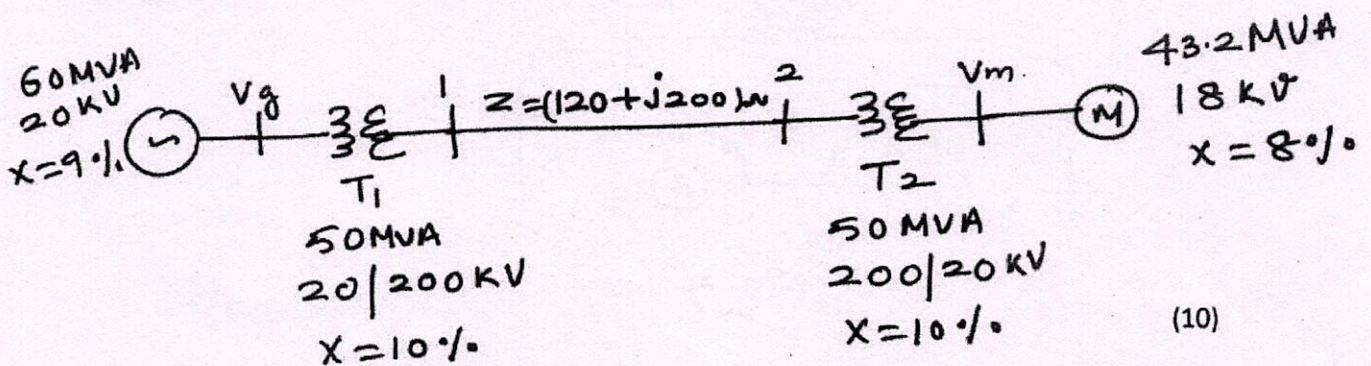3. The three phase power and single line ratings of electric power system as shown in Fig 1. Draw an impedance diagram in per unit on a 100 MVA base. Choose 20 kV as the voltage base for generators.



(10)

Fig 1P.T.O.

(2)

4. In a power system network as shown in Fig 2, determine V_2 using Gauss-Seidel method and perform for two iterations. Also determine S_1 and real and reactive power loss in the line.


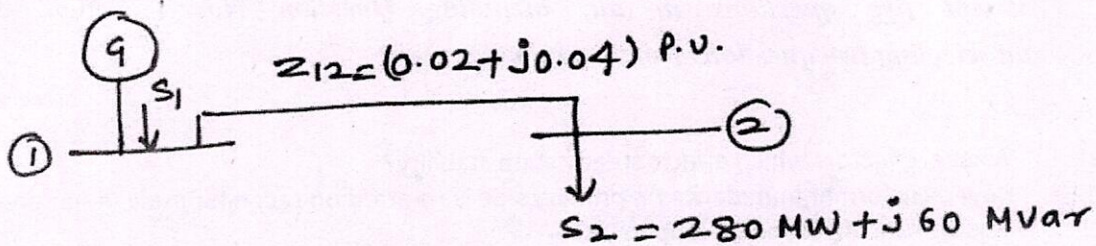


Fig 2

(10)

PART-B

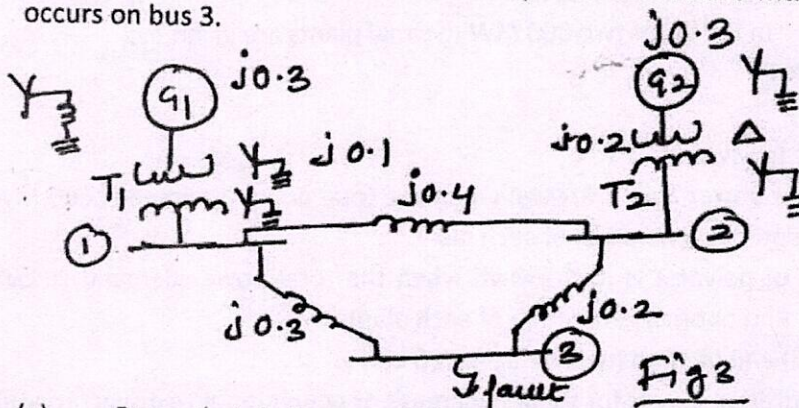5. For a given system as shown in Fig 3, Determine the fault current, bus voltages and line current during the fault when a balanced three phase fault occurs with fault impedance $Z_f = 0.8$ per unit occurs on bus 3.



All values are in Per unit.

Fig 3

(10)

6. (a) Prove that during an unbalanced fault, the three phase power can be represented in symmetrical power components.
 (b) Derive an expression for sequence network connection for double line-to-ground fault.
7. (a) Construct the bus impedance matrix for the network as in Fig 4.

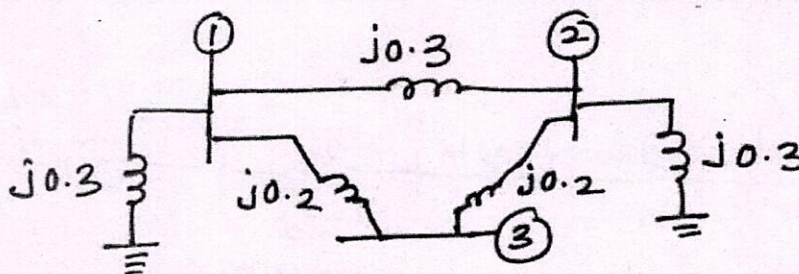


Fig 4

- (b) Discuss zero-sequence impedance of a rotating machinery.

(7,3)

X-X-X